

CS1050 – Computer Organizing and Digital Design

Nano Processor

Table of Contents

Lab Tasks	4
Components.....	8
1. Slow Clock	8
1.1. Design Source File	8
1.2. Elaborate design.....	9
1.3. Simulation File	9
1.4. Timing Diagram.....	11
2. Decoder 3 to 8.....	11
2.1. Design Source File	11
2.2. Elaborate design.....	13
2.3. Simulation File	13
2.4. Timing Diagram.....	15
3. Register.....	16
3.1. Design Source File	16
3.2. Elaborate design.....	17
3.3. Simulation File	17
3.4. Timing Diagram.....	20
4. Register Bank	20
4.1. Design Source File	20
4.2. Elaborate design.....	24
4.3. Simulation File	24
4.4. Timing Diagram.....	27
5. Multiplexer 8 to 1 4bit	27
5.1. Design Source File	27
5.2. Elaborate design.....	29
5.3. Simulation File	29

5.4. Timing Diagram.....	32
6. Multiplexer 2 to 1 4bit.....	32
6.1. Design Source File	32
6.2. Elaborate design.....	34
6.3. Simulation File	34
6.4. Timing Diagram.....	37
7. Program Counter	37
7.1. Design Source File	37
7.2. Elaborate design.....	39
7.3. Simulation File	39
7.4. Timing Diagram.....	42
8. Program Rom.....	42
8.1. Design Source File	42
8.2. Elaborate design.....	44
8.3. Simulation File	44
8.4. Timing Diagram.....	47
9. Adder-Subtractor Unit 4bit	47
9.1. Design Source File	47
9.2. Elaborate design.....	49
9.3. Simulation File	49
9.4. Timing Diagram.....	52
10. Instruction Decoder.....	52
10.1. Design Source File	52
10.2. Elaborate design	55
10.3. Simulation File.....	55
10.4. Timing Diagram.....	58
11. Nano Processor	58
11.1. Design Source File	58
11.2. Elaborate design	65
11.3. Simulation File.....	65
11.4. Timing Diagram.....	68
12. LUT 16_7	68
12.1. Design Source File	68

12.2. Elaborate design	69
12.3. Simulation File.....	70
12.4. Timing Diagram	72
13. Rom Address Select (3 bit adder and Mux 2 way 3 bit)	72
13.1. Design Source File	72
13.2. Elaborate design	74
13.3. Simulation File.....	74
13.4. Timing Diagram.....	77
Optimization	77
Constrain File	79
Workload Distribution	86
Difficulties we face	87
Conclusion	88

Lab Tasks

The primary objective of this lab was to design and implement a simple 4-bit *nanoprocessor* capable of executing a predefined set of instructions. The tasks were divided among team members to ensure collaborative development and integration of multiple components. The following tasks were completed as part of this lab:

1. Design of 4-bit Arithmetic Unit

- Developed a 4-bit adder/subtractor using 2's complement representation.
- Modified the 4-bit Ripple Carry Adder (RCA) from Lab 3 to perform both addition and subtraction based on a control signal.

2. Program Counter and Incrementor

- Implemented a 3-bit Program Counter (PC) using D Flip-Flops with a clear/reset input to allow program restarts.
- Designed a 3-bit adder using a modified 4-bit RCA to increase the PC value on each clock cycle.

3. Multiplexer Design

- Built the following multiplexers using previously developed components:
 - 2-way 3-bit multiplexer
 - 2-way 4-bit multiplexer
 - 8-way 4-bit multiplexer (based on the 8-to-1 multiplexer from Lab 4)
- Explored alternative implementation using tri-state buffers.

4. Register Bank

- Developed a register bank containing eight 4-bit registers (R0–R7).
- Hardcoded R0 to hold the constant value 0.
- Incorporated D Flip-Flops with reset inputs to allow global resetting via a pushbutton.
- Used a 3-to-8 decoder (from Lab 4) for register selection.

5. Program ROM

- Extended the ROM-based LUT from Lab 7 to store machine code instructions.
- Hardcoded the Assembly program into ROM to allow instruction fetching during execution.

6. Instruction Decoder

- Designed the instruction decoder to interpret binary instructions and activate appropriate processor components.
- Ensured precise control signal generation for:
 - Data movement (e.g., MOVI)
 - Arithmetic operations (e.g., ADD, NEG)
 - Conditional jumps (e.g., JZR)
- Used minimal activation logic to prevent conflicting operations during instruction execution.

7. Bus System Integration

- Employed 3-bit, 4-bit, and 12-bit labeled buses to connect major components.
- Streamlined wiring and simplified circuit design using clearly labeled buses such as D(3 downto 0), I(11 downto 0), M(3 downto 0), and R(3 downto 0).

8. Clock and Control Logic


- Integrated a slow clock (2–3 seconds per tick) to observe the execution of each instruction step-by-step.
- Mapped a push button to reset the PC and register bank simultaneously, allowing a fresh start to the program.

9. Team Collaboration

- Tasks were distributed among the five team members to encourage parallel development.
- Regular integration sessions were conducted to ensure seamless merging of independently developed modules.
- Communication and documentation were maintained throughout the development cycle for effective coordination

Instruction Set

Instruction	Description	Format (12-bit instruction)
MOVI R, d	Move immediate value d to register R, i.e., $R \leftarrow d$ $R \in [0, 7], d \in [0, 15]$	1 0 R R R 0 0 0 d d d d
ADD Ra, Rb	Add values in registers Ra and Rb and store the result in Ra, i.e., $Ra \leftarrow Ra + Rb$ $Ra, Rb \in [0, 7]$	0 0 Ra Ra Ra Rb Rb Rb 0 0 0 0
NEG R	2's complement of registers R, i.e., $R \leftarrow -R$ $R \in [0, 7]$	0 1 R R R 0 0 0 0 0 0 0
JZR R, d	Jump if value in register R is 0, i.e., If $R == 0$ $PC \leftarrow d$; Else $PC \leftarrow PC + 1$; $R \in [0, 7], d \in [0, 7]$	1 1 R R R 0 0 0 0 d d d

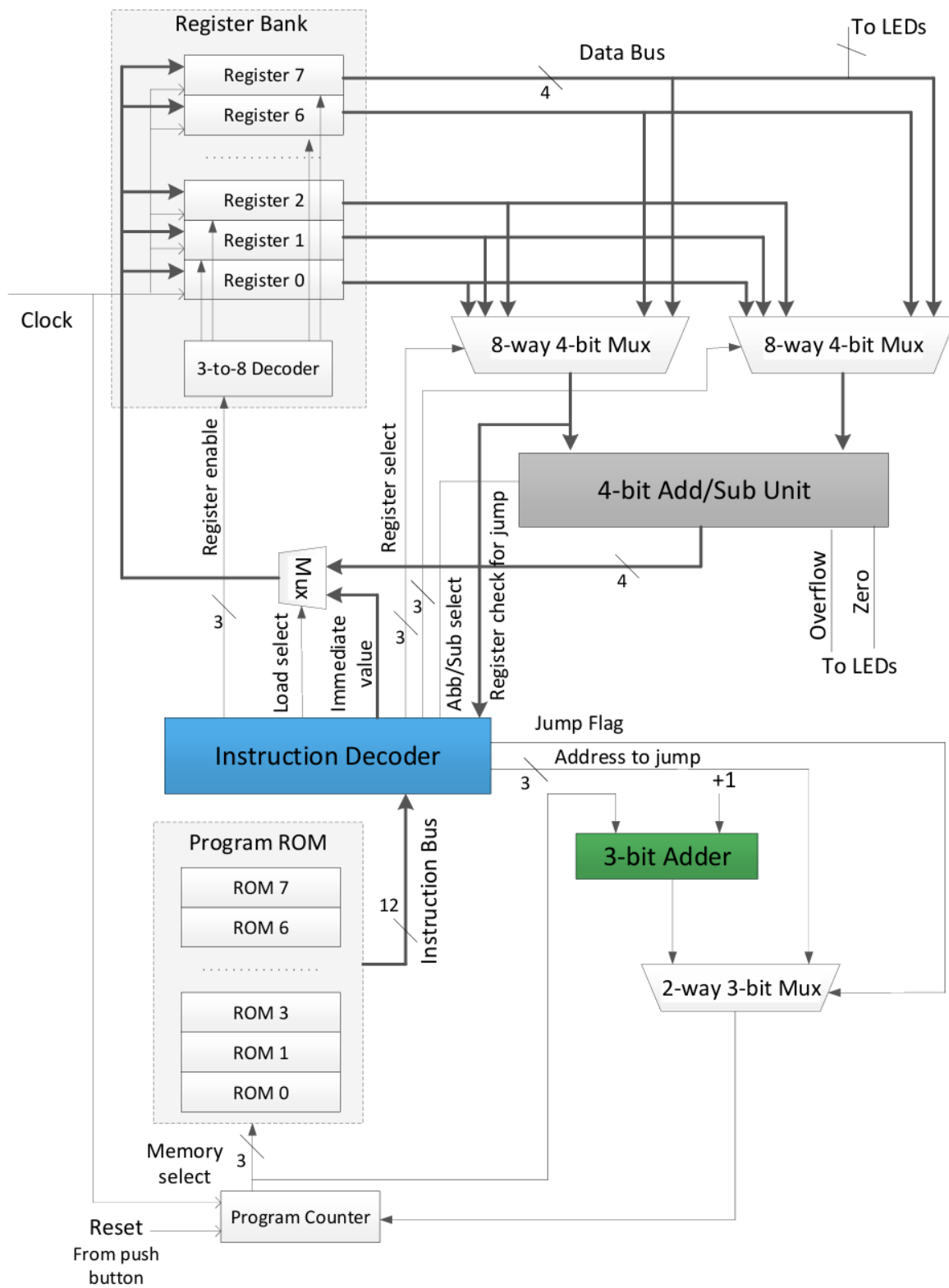

High-level diagram of the *nanoprocessor*.

Components

1. Slow Clock

1.1. Design Source File

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;


-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

-- Entity declaration for Slow_Clk
-- It takes an input clock (Clk_in) and generates a slower clock (Clk_out)
entity Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;      -- Input clock signal
           Clk_out : out STD_LOGIC);   -- Output slower clock signal
end Slow_Clk;

-- Architecture definition for the behavior of Slow_Clk
architecture Behavioral of Slow_Clk is
    -- 26-bit counter =>  $2^{26} = 67,108,864$  (e.g., for 1 Hz from 50 MHz clock)
    signal counter : unsigned(25 downto 0) := (others => '0');
    signal clk_div : STD_LOGIC := '0';

begin
    process(Clk_in)
    begin
        if rising_edge(Clk_in) then
            counter <= counter + 1;
            clk_div <= counter(25); -- Use MSB as divided clock
        end if;
    end process;
    Clk_out <= clk_div;
end Behavioral;
```


1.2. Elaborate design

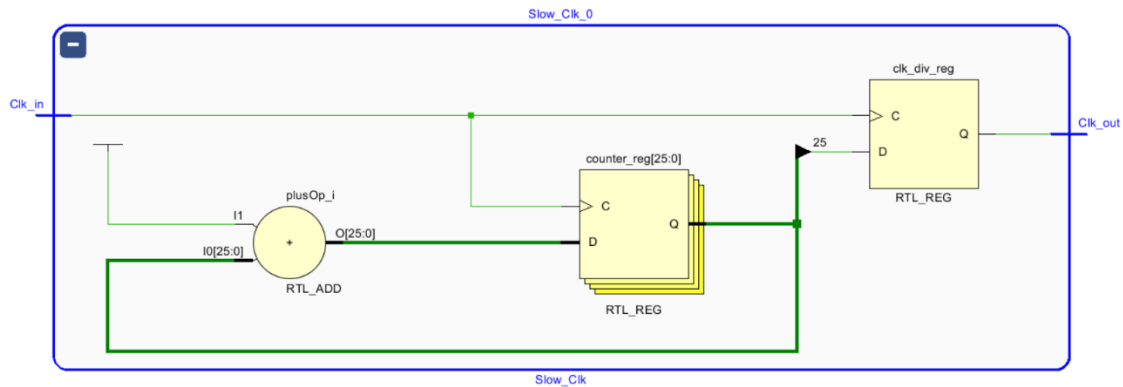

1.3. Simulation File

```
-----  
-- Company:  
-- Engineer:  
--  
-- Create Date: 05/26/2025 06:40:10 AM  
-- Design Name:  
-- Module Name: Sim_Slow_Clk - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool Versions:  
-- Description: Testbench to simulate the Slow_Clk module  
--  
-- Dependencies: Requires the Slow_Clk component  
--  
-- Revision:
```

-- Revision 0.01 - File Created

-- Additional Comments:

--

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Entity declaration for the testbench

entity Sim_Slow_Clk is

-- No ports needed for a testbench

end Sim_Slow_Clk;

-- Behavioral architecture of the testbench

architecture Behavioral of Sim_Slow_Clk is

-- Component declaration of the design under test (Slow_Clk)

component Slow_Clk

Port (

Clk_in : in STD_LOGIC; -- Input clock signal

Clk_out : out STD_LOGIC -- Output slower clock signal

);

end component;

-- Internal signals to connect to the Slow_Clk component

signal Clk_in, Clk_out: STD_LOGIC;

begin

-- Instantiation of the Slow_Clk module

uut: Slow_Clk

port map(

Clk_in => Clk_in,

Clk_out => Clk_out

);

-- Clock generation process

process

begin

-- Generate a clock signal with 10 ns period (5 ns high, 5 ns low)

```

Clk_in <= '0';
wait for 5 ns;

```


```

Clk_in <= '1';
wait for 5 ns;
end process;

```

end Behavioral;

1.4. Timing Diagram

 

2. Decoder 3 to 8

2.1. Design Source File

```

-- Include IEEE standard logic library
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
-- use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
-- library UNISIM;
-- use UNISIM.VComponents.all;

```

```

-- Entity declaration for 3-to-8 decoder
entity Decoder_3_to_8 is
  Port (
    I : in STD_LOGIC_VECTOR (2 downto 0);  -- 3-bit input
    Y : out STD_LOGIC_VECTOR (7 downto 0)  -- 8-bit one-hot output
  );
end Decoder_3_to_8;

-- Behavioral architecture
architecture Behavioral of Decoder_3_to_8 is


begin

  -- Process that triggers whenever input I changes
  process (I) begin
    -- Based on the 3-bit input, assign a corresponding one-hot value to Y
    case (I) is
      when "000" => Y <= "00000001"; -- Output 0 active
      when "001" => Y <= "00000010"; -- Output 1 active
      when "010" => Y <= "00000100"; -- Output 2 active
      when "011" => Y <= "00001000"; -- Output 3 active
      when "100" => Y <= "00010000"; -- Output 4 active
      when "101" => Y <= "00100000"; -- Output 5 active
      when "110" => Y <= "01000000"; -- Output 6 active
      when others => Y <= "10000000"; -- Covers "111" case: Output 7 active
    end case;
  end process;

end Behavioral;

```

2.2. Elaborate design

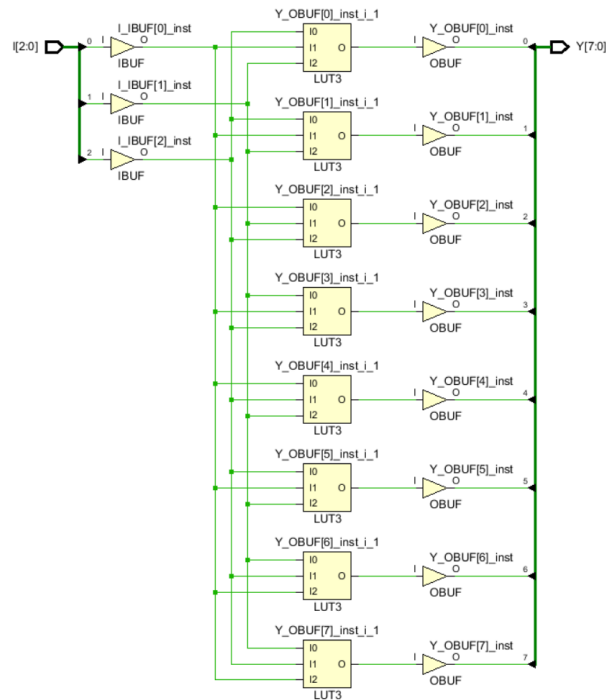

2.3. Simulation File

```
-----  
-- Company:  
-- Engineer:  
--  
-- Create Date: 05/26/2025 06:30:09 AM  
-- Design Name:  
-- Module Name: Sim_Decoder_3_to_8 - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool Versions:  
-- Description: Testbench for 3-to-8 Decoder  
--  
-- Dependencies: Requires 'Decoder_3_to_8' module  
--  
-- Revision:  
-- Revision 0.01 - File Created  
-- Additional Comments:  
--  
-----
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- The entity declaration for the testbench
entity Sim_Decoder_3_to_8 is
-- No ports since this is a testbench
end Sim_Decoder_3_to_8;

-- Architecture of the testbench
architecture Behavioral of Sim_Decoder_3_to_8 is

    -- Component declaration for the 3-to-8 decoder module being tested
    component Decoder_3_to_8
        Port (
            I : in STD_LOGIC_VECTOR (2 downto 0); -- 3-bit binary input
            Y : out STD_LOGIC_VECTOR (7 downto 0) -- 8-bit one-hot output
        );
    end component;

    -- Internal signals to connect to the decoder
    signal I: STD_LOGIC_VECTOR(2 downto 0); -- Input signal to the decoder
    signal Y: STD_LOGIC_VECTOR(7 downto 0); -- Output signal from the decoder

begin
    -- Instantiate the decoder and map internal signals to its ports
    uut: Decoder_3_to_8
        port map (
            I => I,
            Y => Y
        );

    -- Test process to apply input stimuli to the decoder
    process
    begin
        -- Apply all possible 3-bit inputs one by one with 100 ns delay between each
        I <= "000";
        wait for 100 ns;

        I <= "001";
        wait for 100 ns;
    end process
end Behavioral;

```

```
I <= "010";
wait for 100 ns;
```

```
I <= "011";
wait for 100 ns;
```

```
I <= "100";
wait for 100 ns;
```

```
I <= "101";
wait for 100 ns;
```

```
I <= "110";
wait for 100 ns;
```

```
I <= "111";
wait; -- Wait indefinitely after all inputs are applied
end process;
```

end Behavioral;

2.4. Timing Diagram



3. Register

3.1. Design Source File

```
-- Include standard logic library
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Entity declaration for a 4-bit Register
entity Reg is
    Port (
        D : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit data input
        EN : in STD_LOGIC;                    -- Enable signal (active high)
        Clk : in STD_LOGIC;                   -- Clock signal (positive edge triggered)
        Q : out STD_LOGIC_VECTOR (3 downto 0) -- 4-bit data output
    );
end Reg;


-- Behavioral architecture of the 4-bit Register
architecture Behavioral of Reg is

begin

    -- Process triggered on rising edge of the clock
    process(Clk)
    begin
        -- Check for rising edge of the clock
        if rising_edge(Clk) then
            -- Load input D into register only if enable signal is high
            if (EN = '1') then
                Q <= D;
            end if;
        end if;
    end process;

end Behavioral;
```


3.2. Elaborate design

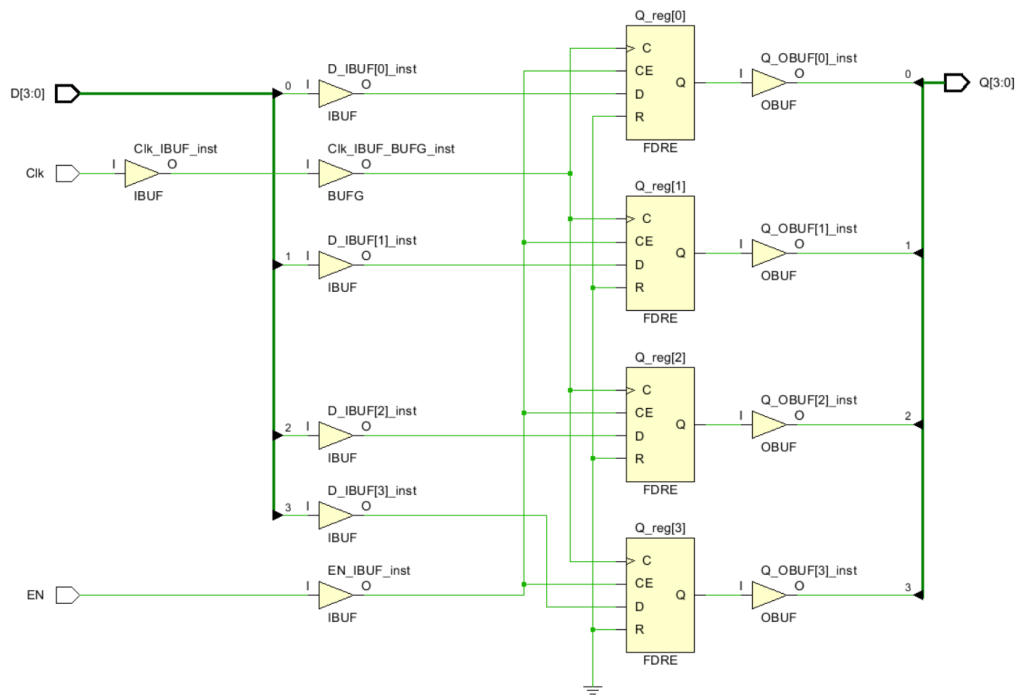

3.3. Simulation File

-- Company:

-- Engineer:

--

-- Create Date: 05/26/2025 06:47:06 AM

-- Design Name:

-- Module Name: Sim_Reg - Behavioral

-- Project Name:

-- Target Devices:

-- Tool Versions:

-- Description: Testbench for a 4-bit register with enable

--

-- Dependencies: Requires 'reg' module

--

-- Revision:

-- Revision 0.01 - File Created

-- Additional Comments:

--

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Entity declaration for the testbench (no ports needed)
entity Sim_Reg is
end Sim_Reg;

-- Architecture for the testbench
architecture Behavioral of Sim_Reg is

    -- Component declaration of the 4-bit register
    component reg
    Port (
        D  : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit data input
        EN : in STD_LOGIC;                    -- Enable signal
        Clk : in STD_LOGIC;                    -- Clock signal
        Q  : out STD_LOGIC_VECTOR (3 downto 0) -- 4-bit data output
    );
    end component;

    -- Signals to connect to the register
    signal D, Q : STD_LOGIC_VECTOR (3 downto 0); -- Input and output data lines
    signal EN, Clk : STD_LOGIC;                -- Enable and Clock signals

begin

    -- Instantiate the register component and map testbench signals to its ports
    uut: reg
    port map (
        D  => D,
        EN => EN,
        Clk => Clk,
        Q  => Q
    );

    -- Clock generation process: produces a clock with 20 ns period
    Clk_process: process
    begin
        Clk <= '0';
        wait for 10 ns;
    end process;
end architecture Behavioral;

```

```

    Clk <= '1';
    wait for 10 ns;
end process;

-- Main stimulus process
Main_process: process
begin
    -- First input (write enabled)
    EN <= '1';          -- Enable the register
    D <= "0110";        -- Set input data to 0110
    wait for 100 ns;    -- Wait to allow multiple clock cycles

    -- Disable writing to register
    EN <= '0';          -- Disable the register
    wait for 100 ns;    -- Output Q should retain previous value


    -- Change input while disabled (Q should not change)
    D <= "1011";        -- New data on input, but EN is low
    wait for 100 ns;

    -- Re-enable writing (register should now load "1011")
    EN <= '1';          -- Enable the register again
    wait;               -- Wait indefinitely for simulation to end
end process;

end Behavioral;

```

3.4. Timing Diagram

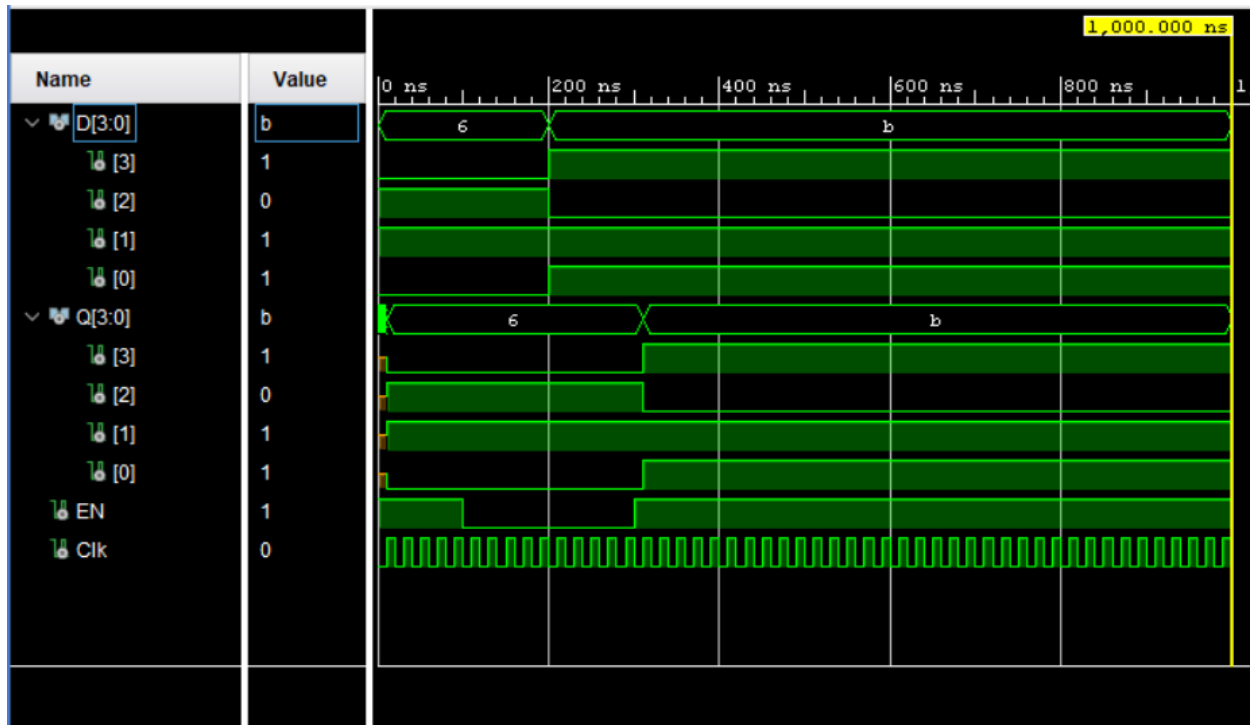

4. Register Bank

4.1. Design Source File

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```

```
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
```

```
-- any Xilinx leaf cells in this code.
```

```
--library UNISIM;
```

```
--use UNISIM.VComponents.all;
```

```
-- Entity declaration for Register Bank with 8 registers
```

```
entity Register_Bank is
```

```
  Port (
```

```
    Reg_EN    : in STD_LOGIC_VECTOR (2 downto 0); -- 3-bit input to select which  
    register to enable
```

```

    Clk      : in STD_LOGIC;           -- Clock signal
    D        : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit data input
    Res      : in STD_LOGIC := '0';    -- Reset signal for all registers
    Reg_0_out : out STD_LOGIC_VECTOR (3 downto 0); -- Output of Register 0
    Reg_1_out : out STD_LOGIC_VECTOR (3 downto 0); -- Output of Register 1
    Reg_2_out : out STD_LOGIC_VECTOR (3 downto 0); -- Output of Register 2
    Reg_3_out : out STD_LOGIC_VECTOR (3 downto 0); -- Output of Register 3
    Reg_4_out : out STD_LOGIC_VECTOR (3 downto 0); -- Output of Register 4
    Reg_5_out : out STD_LOGIC_VECTOR (3 downto 0); -- Output of Register 5
    Reg_6_out : out STD_LOGIC_VECTOR (3 downto 0); -- Output of Register 6
    Reg_7_out : out STD_LOGIC_VECTOR (3 downto 0); -- Output of Register 7
);
end Register_Bank;

```

-- Behavioral architecture of the Register Bank
architecture Behavioral of Register_Bank is

-- Component declaration for 3-to-8 decoder

component Decoder_3_to_8

Port (

 I : in STD_LOGIC_VECTOR (2 downto 0); -- 3-bit input

 Y : out STD_LOGIC_VECTOR (7 downto 0) -- 8 enable outputs

);

end component;

-- Component declaration for 4-bit register

component Reg

Port (

 D : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit data input

 EN : in STD_LOGIC; -- Enable signal

 Clk : in STD_LOGIC; -- Clock signal

 Q : out STD_LOGIC_VECTOR (3 downto 0) -- 4-bit data output

);

end component;

-- Signal to hold outputs from the decoder

signal Y: STD_LOGIC_VECTOR(7 downto 0);

signal EN_1,EN_2,EN_3,EN_4,EN_5,EN_6,EN_7: STD_LOGIC;

signal Input_Vector: STD_LOGIC_VECTOR(3 downto 0);

```
begin
```

```
Input_Vector <= "0000" when (Res = '1') else D;
```

```
-- Instantiate the 3-to-8 decoder to generate enable signals
```

```
Decoder_3_to_8_0: Decoder_3_to_8
```

```
port map(
```

```
    I => Reg_EN, -- Register select input
```

```
    Y => Y      -- Decoder output used to enable one of the 8 registers
```

```
);
```

```
EN_1 <= '1' when (Res = '1') else Y(1);
```

```
EN_2 <= '1' when (Res = '1') else Y(2);
```

```
EN_3 <= '1' when (Res = '1') else Y(3);
```

```
EN_4 <= '1' when (Res = '1') else Y(4);
```

```
EN_5 <= '1' when (Res = '1') else Y(5);
```

```
EN_6 <= '1' when (Res = '1') else Y(6);
```

```
EN_7 <= '1' when (Res = '1') else Y(7);
```

```
-- Instantiate 8 registers, each enabled by a specific bit from decoder output
```

```
Reg_0: Reg
```

```
port map(
```

```
    D => "0000",
```

```
    EN => '1',
```

```
    Clk => Clk,
```

```
    Q => Reg_0_out
```

```
);
```

```
Reg_1: Reg
```

```
port map(
```

```
    D => Input_Vector,
```

```
    EN => EN_1,
```

```
    Clk => Clk,
```

```
    Q => Reg_1_out
```

```
);
```

```
Reg_2: Reg
```

```
port map(
```

```
    D => Input_Vector,
```

```
    EN => EN_2,
```

```
    Clk => Clk,  
    Q => Reg_2_out  
);
```

```
Reg_3: Reg  
  port map(  
    D => Input_Vector,  
    EN => EN_3,  
    Clk => Clk,  
    Q => Reg_3_out  
);
```

```
Reg_4: Reg  
  port map(  
    D => Input_Vector,  
    EN => EN_4,  
    Clk => Clk,  
    Q => Reg_4_out  
);
```

```
Reg_5: Reg  
  port map(  
    D => Input_Vector,  
    EN => EN_5,  
    Clk => Clk,  
    Q => Reg_5_out  
);
```

```
Reg_6: Reg  
  port map(  
    D => Input_Vector,  
    EN => EN_6,  
    Clk => Clk,  
    Q => Reg_6_out  
);
```

```
Reg_7: Reg  
  port map(  
    D => Input_Vector,  
    EN => EN_7,
```


```

    Clk => Clk,
    Q => Reg_7_out
);

```

end Behavioral;

4.2. Elaborate design

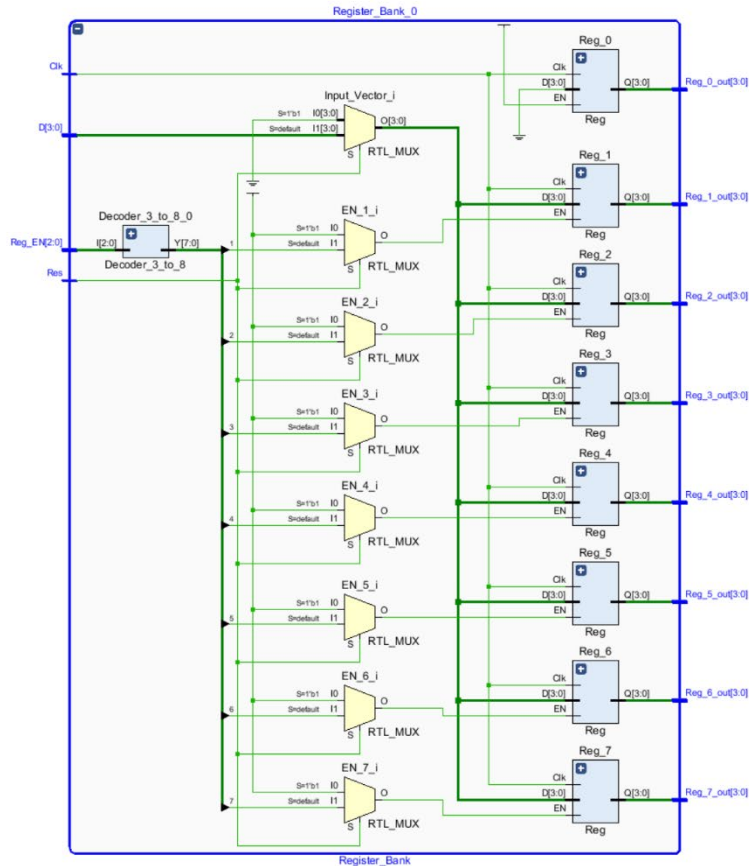

4.3. Simulation File

```

-----
-- Company:
-- Engineer:
--
-- Create Date: 05/05/2025 09:48:57 PM
-- Design Name:
-- Module Name: SIM_Register_Bank - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:

```


-- Description:

--

-- Dependencies:

--

-- Revision:

-- Revision 0.01 - File Created

-- Additional Comments:

--

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating

-- any Xilinx leaf cells in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

-- Testbench entity for Register_Bank (no ports required)

entity SIM_Register_Bank is

-- Port ();

end SIM_Register_Bank;

architecture Behavioral of SIM_Register_Bank is

-- Component declaration for the Register_Bank under test

component Register_Bank

Port (

 Reg_EN : in STD_LOGIC_VECTOR (2 downto 0); -- 3-bit register enable input

 Clk : in STD_LOGIC; -- Clock input

 D : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit data input

 Res : in STD_LOGIC; -- Reset input

 Reg_out: out STD_LOGIC_VECTOR(31 downto 0)

);

end component;

```

-- Internal signals to connect to Register_Bank inputs and outputs
signal Reg_EN: STD_LOGIC_VECTOR(2 downto 0);          -- Register enable select
signal Clk, Res: STD_LOGIC;                          -- Clock and Reset signals
signal D, Reg_0_out, Reg_1_out, Reg_2_out, Reg_3_out, Reg_4_out, Reg_5_out, Reg_6_out,
Reg_7_out: STD_LOGIC_VECTOR(31 downto 0);
signal Reg_out: STD_LOGIC_VECTOR(31 downto 0);
begin

-- Instantiate the Unit Under Test (UUT) Register_Bank
UUT: Register_Bank
  port map(
    Reg_EN => Reg_EN,
    Clk => Clk,
    D => D,
    Res => Res,
    Reg_out => Reg_out
  );

-- Process to drive input stimuli to the Register_Bank
Register_bank_process: process
begin
  Res <= '0';
  Reg_EN <= "000";    -- Enable Register 0
  D <= "0010";        -- Data to be loaded: 2
  wait for 100ns;

  Reg_EN <= "001";    -- Enable Register 1
  D <= "0011";        -- Data to be loaded: 3
  wait for 100ns;

  Reg_EN <= "010";    -- Enable Register 2
  D <= "0000";        -- Data to be loaded: 0
  wait for 100ns;

  Reg_EN <= "011";    -- Enable Register 3
  D <= "0111";        -- Data to be loaded: 7
  wait for 100ns;

  Reg_EN <= "100";    -- Enable Register 4

```

```

D <= "0000";      -- Data to be loaded: 0
wait for 100ns;

Reg_EN <= "101";   -- Enable Register 5
D <= "0011";      -- Data to be loaded: 3
wait for 100ns;

Res <= '1';        -- Activate reset signal
wait;              -- Wait indefinitely

end process;

-- Clock generation process, toggles clock every 10 ns (50 MHz clock)
Clk_process: process
begin
    while true loop
        Clk <= '0';
        wait for 10ns;
        Clk <= '1';
        wait for 10ns;
    end loop;
end process;

end Behavioral;

```

4.4. Timing Diagram

5. Multiplexer 8 to 1 4bit

5.1. Design Source File

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;

```

```

--use UNISIM.VComponents.all;

-- Entity declaration for the 8-way 4-bit multiplexer
entity Mux_8_Way_4_Bit is
  Port (
    I0 : in STD_LOGIC_VECTOR (3 downto 0); -- Input 0
    I1 : in STD_LOGIC_VECTOR (3 downto 0); -- Input 1
    I2 : in STD_LOGIC_VECTOR (3 downto 0); -- Input 2
    I3 : in STD_LOGIC_VECTOR (3 downto 0); -- Input 3
    I4 : in STD_LOGIC_VECTOR (3 downto 0); -- Input 4
    I5 : in STD_LOGIC_VECTOR (3 downto 0); -- Input 5
    I6 : in STD_LOGIC_VECTOR (3 downto 0); -- Input 6
    I7 : in STD_LOGIC_VECTOR (3 downto 0); -- Input 7
    S  : in STD_LOGIC_VECTOR (2 downto 0); -- 3-bit select signal
    Y  : out STD_LOGIC_VECTOR (3 downto 0) -- Output
  );
end Mux_8_Way_4_Bit;


-- Architecture describing the behavior of the multiplexer
architecture Behavioral of Mux_8_Way_4_Bit is

begin
  -- Process sensitive to the select signal S
  process (S)
  begin
    -- Case statement to select the appropriate input based on S
    case S is
      when "000" => Y <= I0; -- Select input I0
      when "001" => Y <= I1; -- Select input I1
      when "010" => Y <= I2; -- Select input I2
      when "011" => Y <= I3; -- Select input I3
      when "100" => Y <= I4; -- Select input I4
      when "101" => Y <= I5; -- Select input I5
      when "110" => Y <= I6; -- Select input I6
      when others => Y <= I7; -- Default: select input I7 for "111" or invalid values
    end case;
  end process;

end Behavioral;

```

5.2. Elaborate design

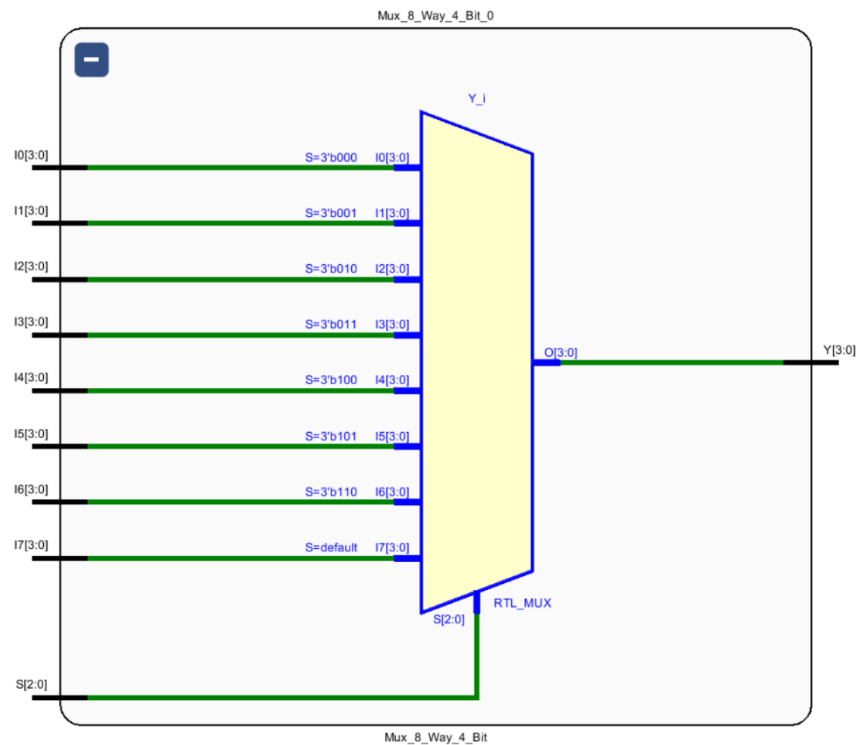

5.3. Simulation File

```
-----  
-- Company:  
-- Engineer:  
--  
-- Create Date: 05/15/2025 07:14:44 PM  
-- Design Name:  
-- Module Name: Sim_Mux_8_Way_4_Bit - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool Versions:  
-- Description:  
--  
-- Dependencies:  
--  
-- Revision:  
-- Revision 0.01 - File Created
```

-- Additional Comments:

--

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating

-- any Xilinx leaf cells in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

entity Sim_Mux_8_Way_4_Bit is

-- Port ();

end Sim_Mux_8_Way_4_Bit;

architecture Behavioral of Sim_Mux_8_Way_4_Bit is

-- Component declaration for the multiplexer

component Mux_8_Way_4_Bit

Port (I0 : in STD_LOGIC_VECTOR (3 downto 0);

I1 : in STD_LOGIC_VECTOR (3 downto 0);

I2 : in STD_LOGIC_VECTOR (3 downto 0);

I3 : in STD_LOGIC_VECTOR (3 downto 0);

I4 : in STD_LOGIC_VECTOR (3 downto 0);

I5 : in STD_LOGIC_VECTOR (3 downto 0);

I6 : in STD_LOGIC_VECTOR (3 downto 0);

I7 : in STD_LOGIC_VECTOR (3 downto 0);

S : in STD_LOGIC_VECTOR (2 downto 0);

Y : out STD_LOGIC_VECTOR (3 downto 0));

end component;

-- Signal declarations for inputs, output, and select lines

signal I0,I1,I2,I3,I4,I5,I6,I7,Y : STD_LOGIC_VECTOR(3 downto 0);

signal S: STD_LOGIC_VECTOR(2 downto 0);

```

begin

-- Instantiate the Mux_8_Way_4_Bit component
UUT: Mux_8_Way_4_Bit
port map(
    I0 => I0,
    I1 => I1,
    I2 => I2,
    I3 => I3,
    I4 => I4,
    I5 => I5,
    I6 => I6,
    I7 => I7,
    S => S,
    Y => Y);

-- Testbench process to apply input stimulus
process begin
    I0 <= "0000"; --0
    I1 <= "0001"; --1
    I2 <= "0010"; --2
    I3 <= "0011"; --3
    I4 <= "0100"; --4
    I5 <= "0101"; --5
    I6 <= "0110"; --6
    I7 <= "0111"; --7

    -- Apply select signal and wait for output
    S <= "000"; -- Select Data from I0
    wait for 100ns;

    S <= "001"; -- Select Data form I1
    wait for 100ns;

    S <= "011"; -- Select Data from I2
    wait for 100ns;


    S <= "111"; -- Select Data from I7
    wait;

```

```
end process;
```

```
end Behavioral;
```

5.4. Timing Diagram

 

6. Multiplexer 2 to 1 4bit

6.1. Design Source File

```
-- Include standard logic library
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Entity declaration for 2-way 4-bit Multiplexer
```

```
entity Mux_2_Way_4_Bit is
```

```
Port (
```

```
    A : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit input A
```

```
    B : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit input B
```

```
    S : in STD_LOGIC; -- Select signal
```

```
    Y : out STD_LOGIC_VECTOR (3 downto 0) -- 4-bit output Y
```

```
);
```



```
end Mux_2_Way_4_Bit;
```

```
-- Behavioral architecture of the multiplexer  
architecture Behavioral of Mux_2_Way_4_Bit is
```

```
-- Declaration of a 1-bit 2-way multiplexer component  
-- This is not instantiated or used in this architecture,  
-- but might be reserved for future structural implementation  
component Mux_2_Way_1_Bit
```

```
    Port (  
        I0 : in STD_LOGIC; -- Input 0  
        I1 : in STD_LOGIC; -- Input 1  
        S  : in STD_LOGIC; -- Select signal  
        Y  : out STD_LOGIC -- Output  
    );
```


```
end component;
```

```
begin
```

```
-- Concurrent assignment:  
-- If S = '1' then output A is assigned to Y  
-- Else output B is assigned to Y  
Y <= A when (S = '1') else B;
```

```
end Behavioral;
```

6.2. Elaborate design

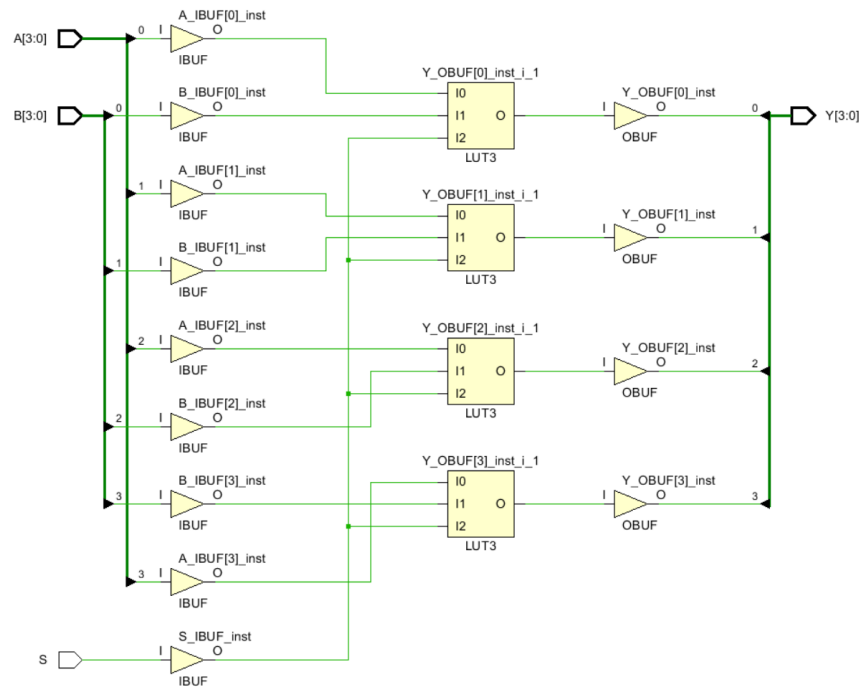

6.3. Simulation File

```
-- Company:
-- Engineer:
--
-- Create Date: 05/15/2025 08:08:53 PM
-- Design Name:
-- Module Name: Sim_Mux_2_Way_4_Bit - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

-- Entity declaration for the testbench of 2-Way 4-Bit Multiplexer
entity Sim_Mux_2_Way_4_Bit is
-- No ports needed for a testbench
end Sim_Mux_2_Way_4_Bit;

architecture Behavioral of Sim_Mux_2_Way_4_Bit is

-- Component declaration for the 2-Way 4-Bit Multiplexer to be tested
component Mux_2_Way_4_Bit
  Port (
    A : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit input A
    B : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit input B
    S : in STD_LOGIC;                -- Select signal
    Y : out STD_LOGIC_VECTOR (3 downto 0) -- 4-bit output
  );
end component;

-- Internal signals to connect to the MUX under test (UUT)
signal A, B, Y : STD_LOGIC_VECTOR(3 downto 0); -- Inputs A, B and output Y
signal S : STD_LOGIC;                -- Select line

begin

-- Instantiate the Unit Under Test (UUT)
UUT: Mux_2_Way_4_Bit
  port map(
    A => A, -- Connect test signal A
    B => B, -- Connect test signal B

```

```

        S => S, -- Connect test select line
        Y => Y  -- Observe output Y
    );


-- Test process to apply stimulus to the UUT
process
begin
    -- Set initial values
    A <= "0101"; -- A = 0101
    B <= "1011"; -- B = 1011

    S <= '0';    -- Select B (S = 0 ? output = B)
    wait for 100ns;

    S <= '1';    -- Select A (S = 1 ? output = A)
    wait;        -- Wait indefinitely (end of simulation)
end process;

end Behavioral;
```

6.4. Timing Diagram

 

7. Program Counter

7.1. Design Source File

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
```

```
-- arithmetic functions with Signed or Unsigned values
```

```
use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
```

```
-- any Xilinx leaf cells in this code.
```

```
--library UNISIM;
```

```
--use UNISIM.VComponents.all;
```


entity ProgramCounter is

```
Port (  
    Clk_in : in STD_LOGIC;           -- Clock input signal  
    Res    : in STD_LOGIC;           -- Asynchronous reset signal (active high)  
    NextVal : in UNSIGNED(2 downto 0); -- Next value to be loaded into the counter (3-  
bit unsigned)  
    Q      : out UNSIGNED(2 downto 0) -- Current output value of the counter (3-bit  
unsigned)  
);  
end ProgramCounter;
```

architecture Behavioral of ProgramCounter is

```
-- Internal signal to hold the current count value  
signal PC : UNSIGNED(2 downto 0) := (others => '0'); -- Initialize PC to 0  
  
begin  
  
    process(Clk_in)  
    begin  
        if rising_edge(Clk_in) then -- Trigger on the rising edge of the clock  
            if Res = '1' then -- If reset is asserted  
                PC <= (others => '0'); -- Reset the program counter to 0  
            else  
                PC <= NextVal; -- Otherwise, load the next value into the counter  
            end if;  
        end if;  
    end process;  
  
    Q <= PC; -- Assign the internal counter value to the output port  
  
end Behavioral;
```

7.2. Elaborate design

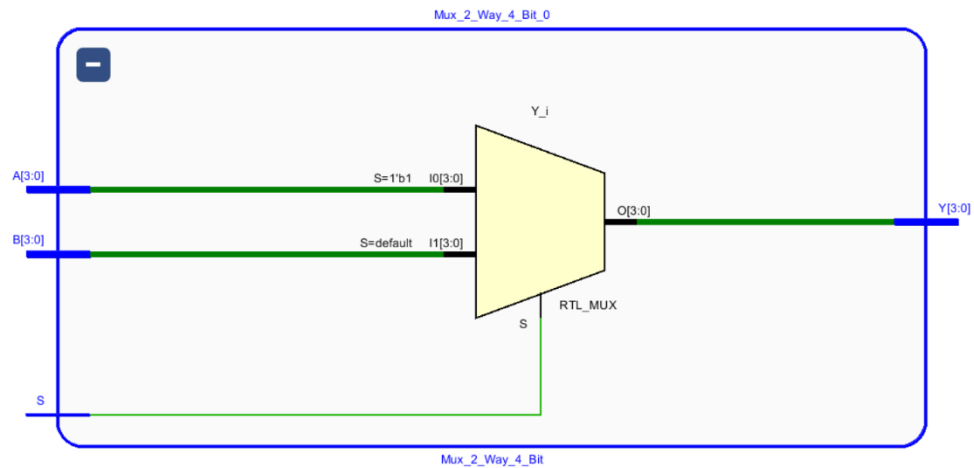

7.3. Simulation File

```
-----  
-- Company:  
-- Engineer:  
--  
-- Create Date: 05/15/2025 08:08:53 PM  
-- Design Name:  
-- Module Name: Sim_Mux_2_Way_4_Bit - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool Versions:  
-- Description:  
--  
-- Dependencies:  
--  
-- Revision:  
-- Revision 0.01 - File Created
```

-- Additional Comments:

--

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating

-- any Xilinx leaf cells in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

-- Entity declaration for the testbench of 2-Way 4-Bit Multiplexer

entity Sim_Mux_2_Way_4_Bit is

-- No ports needed for a testbench

end Sim_Mux_2_Way_4_Bit;

architecture Behavioral of Sim_Mux_2_Way_4_Bit is

-- Component declaration for the 2-Way 4-Bit Multiplexer to be tested

component Mux_2_Way_4_Bit

Port (

A : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit input A

B : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit input B

S : in STD_LOGIC; -- Select signal

Y : out STD_LOGIC_VECTOR (3 downto 0) -- 4-bit output

);

end component;

-- Internal signals to connect to the MUX under test (UUT)

signal A, B, Y : STD_LOGIC_VECTOR(3 downto 0); -- Inputs A, B and output Y

signal S : STD_LOGIC; -- Select line

begin


```

-- Instantiate the Unit Under Test (UUT)
UUT: Mux_2_Way_4_Bit
    port map(
        A => A, -- Connect test signal A
        B => B, -- Connect test signal B
        S => S, -- Connect test select line
        Y => Y  -- Observe output Y
    );

-- Test process to apply stimulus to the UUT
process
begin
    -- Set initial values
    A <= "0101"; -- A = 0101
    B <= "1011"; -- B = 1011


    S <= '0';    -- Select B (S = 0 ? output = B)
    wait for 100ns;

    S <= '1';    -- Select A (S = 1 ? output = A)
    wait;        -- Wait indefinitely (end of simulation)
end process;

end Behavioral;

```

7.4. Timing Diagram

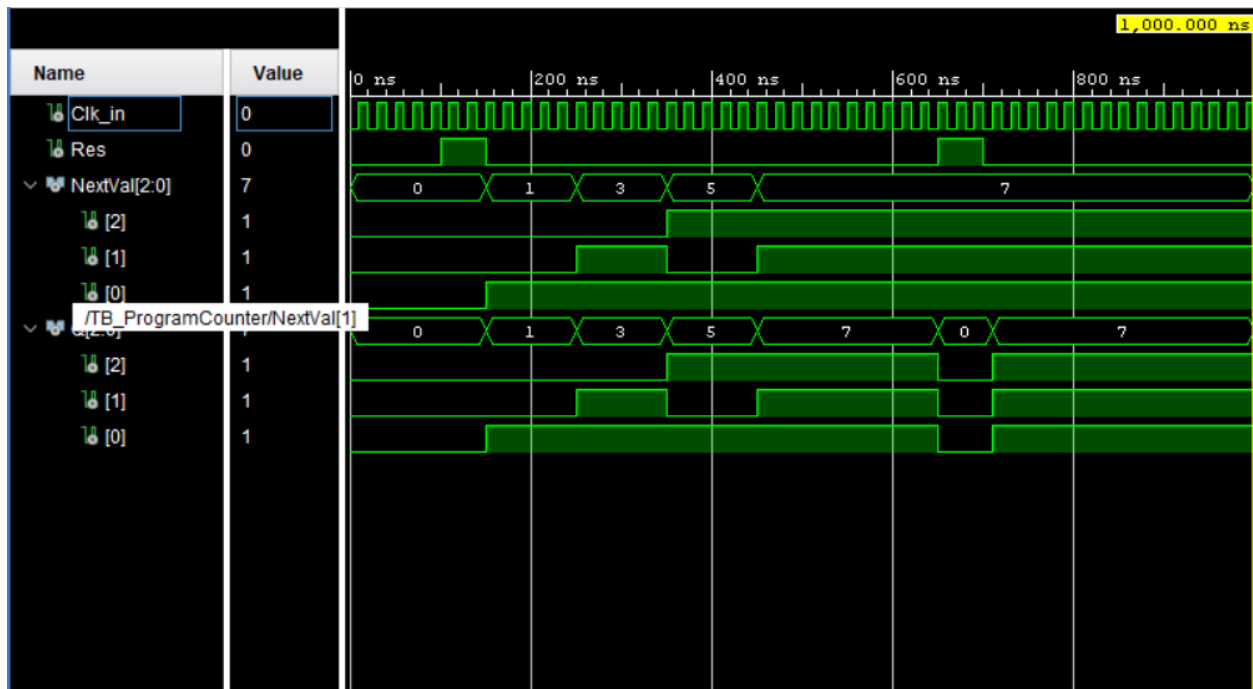

8. Program Rom

8.1. Design Source File

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

-- Entity declaration for a program ROM
-- Takes a 3-bit address input and outputs a 12-bit instruction
entity program_rom is
    Port (
        address : in unsigned (2 downto 0);    -- 3-bit address input
```

```
        instruction : out STD_LOGIC_VECTOR (11 downto 0) -- 12-bit instruction output
    );
end program_rom;
```

-- Architecture defining the behavior of the ROM
architecture Behavioral of program_rom is

-- Define a ROM type as an array of 8 elements, each 12 bits wide
type rom_type is array (0 to 7) of std_logic_vector(11 downto 0);

-- Initialize ROM with predefined instructions


```
signal ROM : rom_type := (
    0 => "100010000001", -- MOVI R1, 1
    1 => "100100000010", -- MOVI R2, 2
    2 => "100110000011", -- MOVI R3, 3
    3 => "101110000000", -- MOVI R7, 0
    4 => "001110010000", -- ADD R7, R1
    5 => "001110100000", -- ADD R7, R2
    6 => "001110110000", -- ADD R7, R3
    7 => "000000000000" -- NOP (or HALT)
);
```

begin

-- Output the instruction at the given address

```
    instruction<= ROM(to_integer(address));
end Behavioral;
```

8.2. Elaborate design

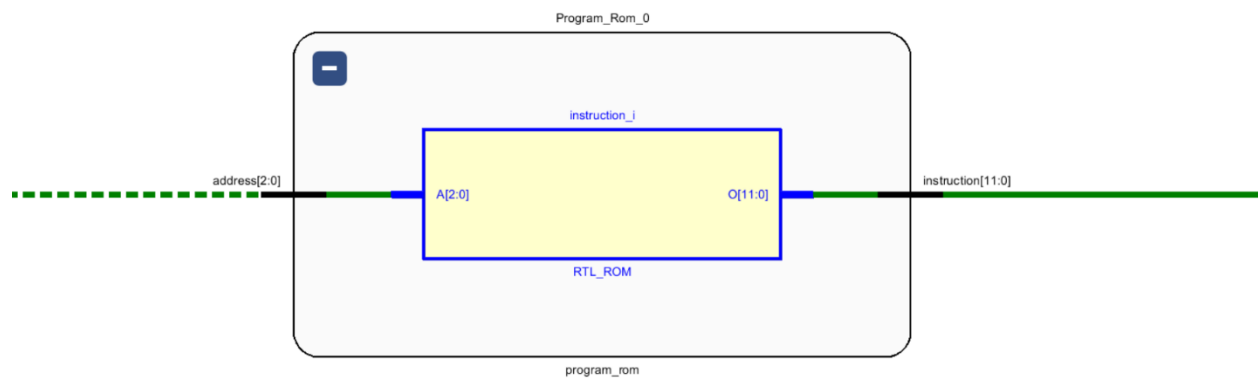

8.3. Simulation File

```
-- Company:
-- Engineer:
--
-- Create Date: 05/11/2025 10:30:23 PM
-- Design Name:
-- Module Name: Sim_program_rom - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
```

-- Additional Comments:

--

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating

-- any Xilinx leaf cells in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

-- Testbench entity for the program_rom

-- No ports are defined since this is a testbench

entity Sim_program_rom is

-- Port ();

end Sim_program_rom;

architecture Behavioral of Sim_program_rom is

-- Declare the component program_rom to be tested

component program_rom

port (

 address : in std_logic_vector (2 downto 0); -- 3-bit address input

 instruction : out std_logic_vector (11 downto 0) -- 12-bit instruction output

);

end component;

-- Signals to connect to the program_rom inputs and outputs

signal address : std_logic_vector (2 downto 0); -- Signal to drive the address input

signal instruction : std_logic_vector (11 downto 0); -- Signal to capture the instruction
output

begin

```

-- Instantiate the Unit Under Test (UUT)
UUT : program_rom
  port map (
    address => address,      -- Connect testbench address signal to UUT input
    instruction => instruction -- Connect UUT instruction output to testbench signal
  );

-- (Note: No test process provided here yet to drive the address signal)
process
begin
  address <= "000"; --- ROM 0
  wait for 20 ns;

  address <= "001"; --- ROM 1
  wait for 20 ns;

  address <= "010"; --- ROM 2
  wait for 20 ns;

  address <= "011"; --- ROM 3
  wait for 20 ns;

  address <= "100"; --- ROM 4
  wait for 20 ns;

  address <= "101"; --- ROM 5
  wait for 20 ns;


  address <= "110"; --- ROM 6
  wait for 20 ns;

  address <= "111"; --- ROM 7
  wait for 20 ns;

  wait;
end process;
end Behavioral;

```

8.4. Timing Diagram

 

9. Adder-Subtractor Unit 4bit

9.1. Design Source File

```
-- Include IEEE standard logic library
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
```

```
-- Entity declaration for a 4-bit Adder/Subtractor Unit
```

```
entity AdderSubtractor4bitUnit is
```

```
    Port (
```

```
        A      : in  STD_LOGIC_VECTOR(3 downto 0); -- 4-bit input A
```

```
        B      : in  STD_LOGIC_VECTOR(3 downto 0); -- 4-bit input B
```

```
        ADD_SUB : in  STD_LOGIC;                    -- Operation select: '0' for add, '1' for subtract
```

```
        RESULT  : out STD_LOGIC_VECTOR(3 downto 0); -- 4-bit result output
```

```
        C_OUT   : out STD_LOGIC;                    -- Carry-out (not used in this architecture)
```

```
        OVERFLOW : out STD_LOGIC;                  -- Overflow flag output from RCA_4
```

```
        ZERO    : out STD_LOGIC                    -- Zero flag: '1' if result is all zeros
```

```
    );
```

```
end AdderSubtractor4bitUnit;
```

```
-- Architecture definition using a 4-bit Ripple Carry Adder component
```

```
architecture Behavioral of AdderSubtractor4bitUnit is
```

```

-- Internal signals
signal A_mod : STD_LOGIC_VECTOR(3 downto 0); -- Modified A input (inverted for
subtraction)
signal B_mod : STD_LOGIC_VECTOR(3 downto 0); -- Modified B input (zero for
subtraction)
signal S    : STD_LOGIC_VECTOR(4 downto 0); -- Output from RCA_4, 5 bits to include
carry/overflow
signal temp_sum : unsigned(4 downto 0);    -- Unsigned 5-bit internal sum to hold carry

begin

-- Logic for operand selection:
-- If ADD_SUB = '0' ? addition: A_mod = A, B_mod = B
-- If ADD_SUB = '1' ? subtraction: A_mod = NOT A (two's complement), B_mod = "0000"
A_mod <= A when (ADD_SUB = '0') else not(A); -- Invert A for subtraction
B_mod <= B when (ADD_SUB = '0') else (others => '0'); -- Set B to zero in subtraction

-- Perform the operation:
-- For addition: A + B
-- For subtraction: NOT A + 0 + 1 (2's complement of A), simulating -A
temp_sum <= ('0' & unsigned(A_mod)) + unsigned(B_mod) + ("0000" & ADD_SUB);

-- Assign calculated value to output signal S
S <= STD_LOGIC_VECTOR(temp_sum);

-- Set 4-bit RESULT from lower 4 bits of S
RESULT <= S(3 downto 0);

-- ZERO flag: '1' if result is all zeros, else '0'
ZERO <= not (S(0) OR S(1) OR S(2) OR S(3));


-- Overflow is indicated by the 5th bit (MSB) of the sum
OVERFLOW <= S(4);

-- Note: C_OUT is declared in the port but is not assigned or used in this architecture

end Behavioral;

```


9.2. Elaborate design

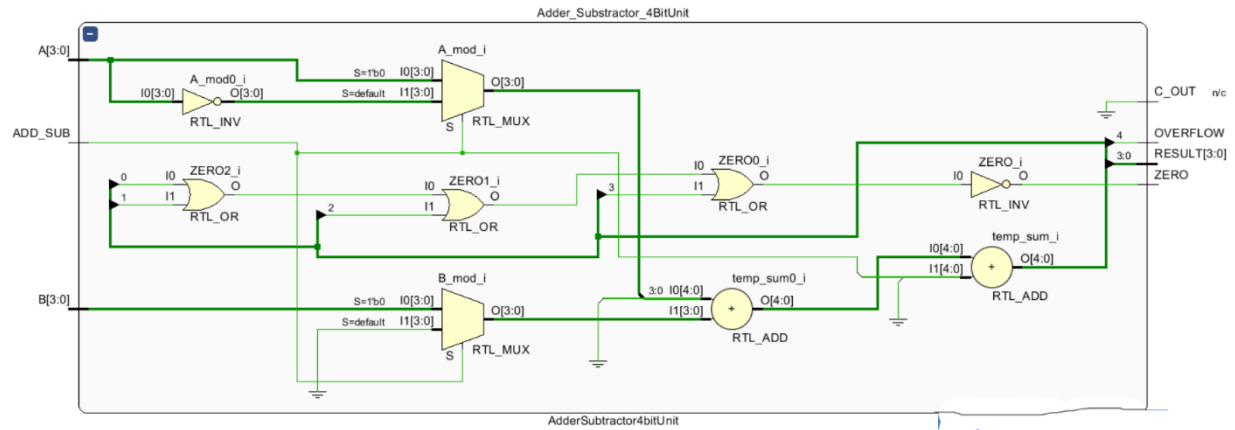

9.3. Simulation File

```
-- Company:
-- Engineer:
--
-- Create Date: 05/14/2025 08:28:12 PM
-- Design Name:
-- Module Name: TB_AdderSubtractor4bitUnit - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
```

-- Additional Comments:

--

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating

-- any Xilinx leaf cells in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

entity TB_AdderSubtractor4bitUnit is

-- Port ();

end TB_AdderSubtractor4bitUnit;

architecture Behavioral of TB_AdderSubtractor4bitUnit is

component AdderSubtractor4bitUnit

Port (

A : in STD_LOGIC_VECTOR(3 downto 0);

B : in STD_LOGIC_VECTOR(3 downto 0);

ADD_SUB : in STD_LOGIC;

RESULT : out STD_LOGIC_VECTOR(3 downto 0);

OVERFLOW : out STD_LOGIC;

ZERO : out STD_LOGIC

);

end component;

-- Signals for test

signal A, B : STD_LOGIC_VECTOR(3 downto 0);

signal ADD_SUB : STD_LOGIC;

signal RESULT : STD_LOGIC_VECTOR(3 downto 0);

signal C_OUT : STD_LOGIC;

signal OVERFLOW : STD_LOGIC;

signal ZERO : STD_LOGIC;

```
begin
```

```
UUT: AdderSubtractor4bitUnit
```

```
port map (
```

```
  A    => A,
```

```
  B    => B,
```

```
  ADD_SUB => ADD_SUB,
```

```
  RESULT => RESULT,
```

```
  OVERFLOW => OVERFLOW,
```

```
  ZERO    => ZERO
```

```
);
```

```
-- Test process
```

```
process
```

```
begin
```

```
  -- Test case 1: 5 + 7
```

```
  A <= "0101"; -- 5
```

```
  B <= "0111"; -- 7
```

```
  ADD_SUB <= '0'; -- Add
```

```
  wait for 10 ns;-- 1100
```

```
  A <= "0111"; -- 7
```

```
  B <= "0011"; -- 3
```

```
  ADD_SUB <= '1'; -- Subtract
```

```
  wait for 10 ns; --1001
```

```
  A <= "0010"; -- 2
```

```
  B <= "0101"; -- 5
```

```
  ADD_SUB <= '1'; -- Subtract
```

```
  wait for 10 ns;--1110
```

```
  -- Test case 4: 8 + 8 (expect overflow)
```

```
  A <= "1000"; -- 8
```

```
  B <= "1000"; -- 8
```

```
  ADD_SUB <= '0';
```

```
  wait for 10 ns;--0000
```

```


A <= "0100"; -- 4
B <= "0100"; -- 4
ADD_SUB <= '1';-- Subtract
wait for 10 ns; --1100

    wait; -- Stop simulation
end process;

end Behavioral;

```

9.4. Timing Diagram

 

10. Instruction Decoder

10.1. Design Source File

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

-- Entity declaration for InstructionDecoder
-- Decodes a 12-bit instruction bus into control signals and register selections
entity InstructionDecoder is
    Port (
        InstructionBus : in STD_LOGIC_VECTOR (11 downto 0); -- 12-bit instruction input
        RegisterCheck : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit input for register
condition checking
        Reg_EN : out STD_LOGIC_VECTOR (2 downto 0); -- 3-bit output for register select 1
        RegSelect_A : out STD_LOGIC_VECTOR (2 downto 0); -- 3-bit output for register
select 2
        RegSelect_B : out STD_LOGIC_VECTOR (2 downto 0); -- 3-bit output for register
select 3
        LoadSelect : out STD_LOGIC; -- Control signal for load selection
        ImmediateValue : out STD_LOGIC_VECTOR (3 downto 0); -- 4-bit immediate value
output
        OperationSelect : out STD_LOGIC; -- Control signal for operation selection
        JumpFlag: out STD_LOGIC; -- Flag indicating if jump instruction is
active
        JumpAddress: out unsigned(2 downto 0) -- 3-bit jump address output
    );
end InstructionDecoder;

architecture Behavioral of InstructionDecoder is

-- Signal to hold the 2-bit opcode extracted from the instruction bus
    signal Opcode : STD_LOGIC_VECTOR(1 downto 0);
begin

    process(InstructionBus, RegisterCheck)
        variable opcode_var : STD_LOGIC_VECTOR(1 downto 0);

```

```

begin
  opcode_var := InstructionBus(11 downto 10);

  -- Default assignments:
  RegSelect_A <= InstructionBus(9 downto 7);
  RegSelect_B <= InstructionBus(6 downto 4);
  ImmediateValue <= InstructionBus(3 downto 0);
  JumpAddress <= unsigned(InstructionBus(2 downto 0));
  OperationSelect <= InstructionBus(10);
  LoadSelect <= not InstructionBus(11);
  JumpFlag <= '0';
  Reg_EN <= InstructionBus(9 downto 7);

  case opcode_var is
    when "10" => -- MOVI
      Reg_EN <= InstructionBus(9 downto 7);
      -- LoadSelect = 0 (already set above)

    when "00" => -- ADD
      Reg_EN <= InstructionBus(9 downto 7);
      -- LoadSelect = 1 (already set above)

    when "01" => -- NEG
      Reg_EN <= InstructionBus(9 downto 7);
      -- OperationSelect already set


    when "11" => -- JZR
      if RegisterCheck = "0000" then
        JumpFlag <= '1';
      else
        JumpFlag <= '0';
      end if;
      Reg_EN <= "000"; -- prevent register writes during jump

    when others =>
      Reg_EN <= "000";
      JumpFlag <= '0';
  end case;
end process;

```

end Behavioral;

10.2. Elaborate design

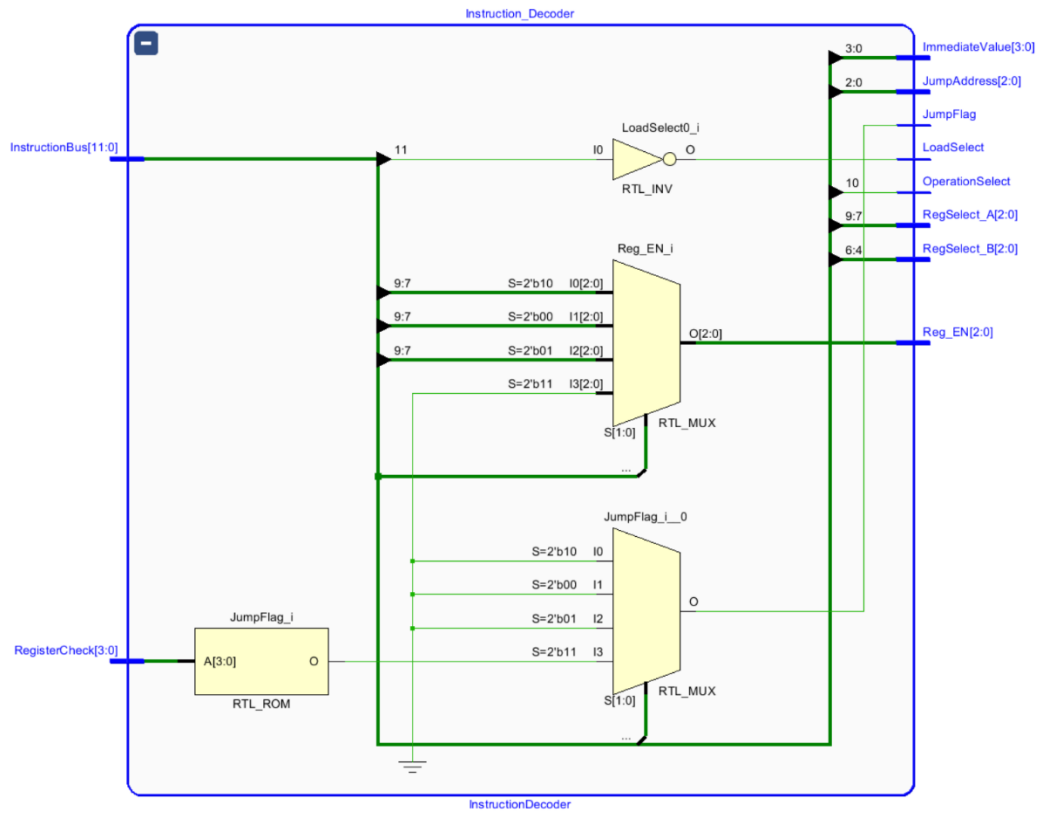

10.3. Simulation File

-- Company:
-- Engineer:
--
-- Create Date: 05/14/2025 01:38:50 PM
-- Design Name:
-- Module Name: Sim_Instruction_Decoder - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:

```
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```

```
entity Sim_Instruction_Decoder is
-- Port ( );
end Sim_Instruction_Decoder;
```

```
architecture Behavioral of Sim_Instruction_Decoder is
```

```
-- Component declaration for the InstructionDecoder to be tested
component InstructionDecoder
  Port (
    InstructionBus : in STD_LOGIC_VECTOR (11 downto 0);  -- 12-bit instruction input
    RegisterCheck : in STD_LOGIC_VECTOR (3 downto 0);    -- 4-bit register check
input
    Reg_EN : out STD_LOGIC_VECTOR (2 downto 0);          -- Register Enable
    RegSelect_A : out STD_LOGIC_VECTOR (2 downto 0);      -- Register select output A
    RegSelect_B : out STD_LOGIC_VECTOR (2 downto 0);      -- Register select output B
    LoadSelect : out STD_LOGIC;                          -- Load select control signal
    ImmediateValue : out STD_LOGIC_VECTOR (3 downto 0);   -- Immediate value
output
    OperationSelect : out STD_LOGIC;                      -- Operation select control signal
    JumpFlag: out STD_LOGIC;                             -- Jump flag output
```



```

        JumpAddress: out STD_LOGIC_VECTOR(2 downto 0)        -- Jump address output
    );
end component;

-- Signals to connect to InstructionDecoder inputs and outputs
signal InstructionBus: STD_LOGIC_VECTOR(11 downto 0);
signal RegisterCheck, ImmediateValue : STD_LOGIC_VECTOR(3 downto 0);
signal Reg_EN, RegSelect_A, RegSelect_B, JumpAddress: STD_LOGIC_VECTOR(2
downto 0);
signal LoadSelect, OperationSelect, JumpFlag: STD_LOGIC;

begin

-- Instantiate the Unit Under Test (UUT)
UUT : InstructionDecoder
port Map(
    InstructionBus => InstructionBus,
    RegisterCheck => RegisterCheck,
    Reg_EN => Reg_EN,
    RegSelect_A => RegSelect_A,
    RegSelect_B => RegSelect_B,
    LoadSelect => LoadSelect,
    ImmediateValue => ImmediateValue,
    OperationSelect => OperationSelect,
    JumpFlag => JumpFlag,
    JumpAddress => JumpAddress);

-- Test process to drive different instruction inputs and observe outputs
process
begin
    -- Test case 1: MOVI R1, 10 or similar instruction
    InstructionBus <= "100010001010";
    wait for 100 ns;

    -- Test case 2: NEG or arithmetic operation
    InstructionBus <= "010100000000";
    wait for 100 ns;

    -- Test case 3: ADD or other arithmetic instruction
    InstructionBus <= "000100010000";

```

```

wait for 100 ns;


-- Test case 4: Jump instruction with RegisterCheck zero (enabling jump)
InstructionBus <= "110010000011";
RegisterCheck <= "0000"; -- Must be set to enable jump in decoder
wait for 100 ns;

-- Test case 5: NOP or default instruction
InstructionBus <= "000000000000";
wait; -- Wait indefinitely to end simulation
end process;

end Behavioral;

```

10.4. Timing Diagram

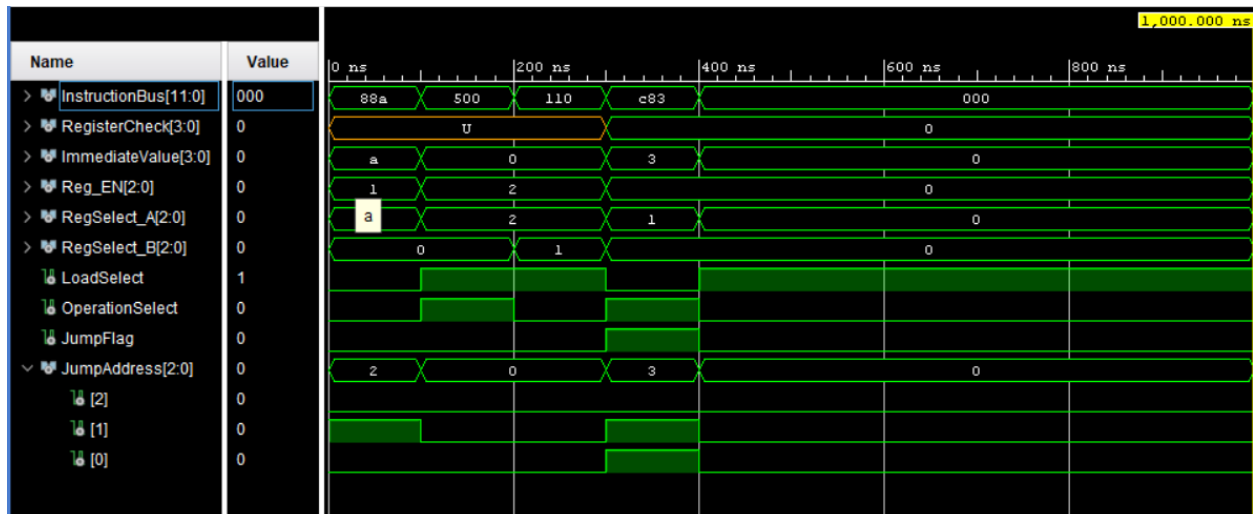

11. Nano Processor

11.1. Design Source File

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

-- Entity declaration for the Nano Processor
entity Nano_Processor is
    Port (
        Res, Clk : in STD_LOGIC;          -- Reset and Clock inputs

```

```

    Reg_7_out : out STD_LOGIC_VECTOR (3 downto 0); -- Output of Register 7
    Overflow, Zero: out STD_LOGIC;                -- ALU status flags: Overflow and Zero
    Display_7_Segment: out STD_LOGIC_VECTOR(6 downto 0); -- Output signals to 7-
segment display (7 segments)
    an: out STD_LOGIC_VECTOR(3 downto 0)           -- Anode control for 4-digit 7-
segment display (active low)
);
end Nano_Processor;

```

architecture Behavioral of Nano_Processor is

```

-- Register bank: 8 registers, each 4-bit wide
component Register_Bank
Port (
    Reg_EN    : in STD_LOGIC_VECTOR (2 downto 0); -- 3-bit register enable address
(select which register to write)
    Clk       : in STD_LOGIC;                -- Clock signal
    D         : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit data input to registers
    Res       : in STD_LOGIC := '0';         -- Reset signal to reset all registers
    Reg_0_out  : out STD_LOGIC_VECTOR (3 downto 0); -- Outputs for each register (0 to
7)
    Reg_1_out  : out STD_LOGIC_VECTOR (3 downto 0);
    Reg_2_out  : out STD_LOGIC_VECTOR (3 downto 0);
    Reg_3_out  : out STD_LOGIC_VECTOR (3 downto 0);
    Reg_4_out  : out STD_LOGIC_VECTOR (3 downto 0);
    Reg_5_out  : out STD_LOGIC_VECTOR (3 downto 0);
    Reg_6_out  : out STD_LOGIC_VECTOR (3 downto 0);
    Reg_7_out  : out STD_LOGIC_VECTOR (3 downto 0)
);
end component;

```

```

-- ALU: 4-bit Adder/Subtractor Unit
component AdderSubtractor4bitUnit

```

```

Port (
    A, B      : in STD_LOGIC_VECTOR(3 downto 0); -- Two 4-bit operands
    ADD_SUB   : in STD_LOGIC;                    -- Operation select: 0 for add, 1 for subtract
    RESULT    : out STD_LOGIC_VECTOR(3 downto 0); -- 4-bit result output
    OVERFLOW  : out STD_LOGIC;                    -- Overflow flag output
    ZERO      : out STD_LOGIC                     -- Zero flag output
);

```

end component;

-- 2-to-1 multiplexer for 4-bit data input selection

component Mux_2_Way_4_Bit

Port (

A, B : in STD_LOGIC_VECTOR (3 downto 0); -- Two 4-bit inputs

S : in STD_LOGIC; -- Select signal: 0 selects A, 1 selects B

Y : out STD_LOGIC_VECTOR (3 downto 0) -- Output of the mux

);

end component;

-- 2-to-1 multiplexer for 3-bit addresses (used for selecting ROM address)

component Rom_Address_Select

Port (

A, B : in unsigned(2 downto 0); -- Two 3-bit address inputs

S : in STD_LOGIC; -- Select signal: 0 selects A, 1 selects B

Y : out unsigned (2 downto 0) -- Output selected address

);

end component;

-- 8-to-1 multiplexer for selecting one of 8 registers (4-bit each)

component Mux_8_Way_4_Bit

Port (

I0, I1, I2, I3, I4, I5, I6, I7 : in STD_LOGIC_VECTOR (3 downto 0); -- Inputs from all 8 registers

S : in STD_LOGIC_VECTOR (2 downto 0); -- 3-bit select to choose one register

Y : out STD_LOGIC_VECTOR (3 downto 0) -- Output selected register data

);

end component;

-- Instruction decoder: decodes 12-bit instruction into control signals

component InstructionDecoder

Port (

InstructionBus : in STD_LOGIC_VECTOR (11 downto 0); -- 12-bit instruction input

RegisterCheck : in STD_LOGIC_VECTOR (3 downto 0); -- Data from selected register A (for instruction checking)

Reg_EN : out STD_LOGIC_VECTOR (2 downto 0); -- Register to write enable (3 bits)

```

        RegSelect_A   : out STD_LOGIC_VECTOR (2 downto 0); -- Register A selector (3 bits)
        RegSelect_B   : out STD_LOGIC_VECTOR (2 downto 0); -- Register B selector (3
bits)
        LoadSelect    : out STD_LOGIC;                    -- Select load source (ALU result or
immediate)
        ImmediateValue : out STD_LOGIC_VECTOR (3 downto 0); -- Immediate 4-bit value
from instruction
        OperationSelect : out STD_LOGIC;                  -- ALU operation select (Add/Sub)
        JumpFlag        : out STD_LOGIC;                  -- Jump flag signal
        JumpAddress     : out unsigned(2 downto 0)         -- Jump address for PC
    );
end component;

-- Program Counter: holds current instruction address (3-bit)
component ProgramCounter
    Port (
        Clk_in  : in STD_LOGIC;                -- Clock input
        Res     : in STD_LOGIC;                -- Reset signal
        NextVal : in unsigned (2 downto 0);      -- Next address input
        Q       : out unsigned (2 downto 0)     -- Current address output
    );
end component;

-- Clock divider to slow down system clock for visibility / timing reasons
component Slow_Clk
    Port (
        Clk_in  : in STD_LOGIC;                -- Fast clock input
        Clk_out : out STD_LOGIC                 -- Slower clock output
    );
end component;

-- 3-bit adder that adds 1 to the current PC value (used for PC increment)
component adder_3bit
    Port (
        INPUT  : in unsigned (2 downto 0);      -- Input 3-bit number
        OUTPUT : out unsigned (2 downto 0)      -- Output incremented by 1
    );
end component;

-- ROM: Program memory holding instructions (8 locations, 12-bit wide instructions)

```

```

component program_rom
  Port (
    address    : in unsigned (2 downto 0);      -- 3-bit address input
    instruction : out STD_LOGIC_VECTOR (11 downto 0) -- 12-bit instruction output
  );
end component;

-- Lookup table to convert 4-bit binary value to 7-segment display pattern
component LUT_16_7
  Port (
    address : in STD_LOGIC_VECTOR (3 downto 0);      -- 4-bit input value
    data    : out STD_LOGIC_VECTOR (6 downto 0)      -- 7-bit segment pattern output
  );
end component;

-- Internal signals used for interconnecting components
signal Clk_out, Jump_Flag, LoadSelect, OperationSelect : STD_LOGIC;
signal Instruction_Bus_1 : STD_LOGIC_VECTOR(11 downto 0);
signal Next_Rom_Address, Rom_Address_Add, Rom_Address, Jump_Address : unsigned(2
downto 0);
signal Reg_EN, RegSelect_A, RegSelect_B : STD_LOGIC_VECTOR(2 downto 0);
signal Reg_A, Reg_B, ImmediateValue, Result, Value : STD_LOGIC_VECTOR(3 downto 0);
signal Reg_0, Reg_1, Reg_2, Reg_3, Reg_4, Reg_5, Reg_6, Reg_7 :
STD_LOGIC_VECTOR(3 downto 0);

begin

  -- Instantiate the slow clock generator to reduce clock speed for timing
  Slow_Clk_0: Slow_Clk
  port map(Clk_in => Clk, Clk_out => Clk_out);

  -- Instantiate the Program Counter with slow clock and reset
  Program_Counter: ProgramCounter
  port map(Clk_in => Clk_out, Res => Res, NextVal => Next_Rom_Address, Q =>
Rom_Address);

  -- PC + 1 adder to calculate next sequential instruction address (currently commented out)
  --Adder_3_Bit: adder_3bit
  --port map(INPUT => Rom_Address, OUTPUT => Rom_Address_Add);

```

```

-- Multiplexer to select between jump address and next sequential PC address
Rom_Address_Select_0: Rom_Address_Select
port map(A => Jump_Address, B => Rom_Address, S => Jump_Flag, Y =>
Next_Rom_Address);

-- Instruction memory ROM: fetch instruction based on current PC
Program_Rom_0: Program_Rom
port map(address => Rom_Address, Instruction => Instruction_Bus_1);

-- Instruction decoder: decode instruction into control signals and immediate values
Instruction_Decoder: InstructionDecoder
port map(
    InstructionBus => Instruction_Bus_1,
    RegisterCheck => Reg_A,
    Reg_EN => Reg_EN,
    RegSelect_A => RegSelect_A,
    RegSelect_B => RegSelect_B,
    LoadSelect => LoadSelect,
    ImmediateValue => ImmediateValue,
    OperationSelect => OperationSelect,
    JumpFlag => Jump_Flag,
    JumpAddress => Jump_Address);

-- Register bank: 8 registers, load enabled by Reg_EN on rising clock edge
Register_Bank_0: Register_Bank
port map(
    Reg_EN => Reg_EN,
    Clk => Clk_out,
    D => Value,
    Res => Res,
    Reg_0_out => Reg_0, Reg_1_out => Reg_1, Reg_2_out => Reg_2, Reg_3_out =>
Reg_3, Reg_4_out => Reg_4,
    Reg_5_out => Reg_5, Reg_6_out => Reg_6, Reg_7_out => Reg_7);

-- Mux to select either ALU Result or Immediate value for loading into register
Mux_2_Way_4_Bit_0: Mux_2_Way_4_Bit
port map(A => Result, B => ImmediateValue, S => LoadSelect, Y => Value);

-- Mux to select Register A data based on RegSelect_A (used as ALU input and decoder input)
Mux_8_Way_4_Bit_0: Mux_8_Way_4_Bit

```

```

port map(
    I0 => Reg_0, I1 => Reg_1, I2 => Reg_2, I3 => Reg_3,
    I4 => Reg_4, I5 => Reg_5, I6 => Reg_6, I7 => Reg_7,
    S => RegSelect_A, Y => Reg_A);

-- Mux to select Register B data based on RegSelect_B (used as ALU input)
Mux_8_Way_4_Bit_1: Mux_8_Way_4_Bit
port map(
    I0 => Reg_0, I1 => Reg_1, I2 => Reg_2, I3 => Reg_3,
    I4 => Reg_4, I5 => Reg_5, I6 => Reg_6, I7 => Reg_7,
    S => RegSelect_B, Y => Reg_B);

-- ALU: 4-bit Adder/Subtractor unit performs operation on Reg_A and Reg_B
Adder_Subtractor_4BitUnit: AdderSubtractor4bitUnit
port map(
    A => Reg_A, B => Reg_B, ADD_SUB => OperationSelect,
    Result => Result, OverFlow => OverFlow, ZERO => Zero);

-- Lookup table converts 4-bit Register 7 output into 7-segment display encoding
LUT_16_7_0: LUT_16_7
port map(address => Reg_7, data => Display_7_Segment);


-- Output the contents of Register 7 externally
Reg_7_out <= Reg_7;

-- Enable only the first digit of the 7-segment display (active low)
an <= "1110";

end Behavioral;

```


11.2. Elaborate design

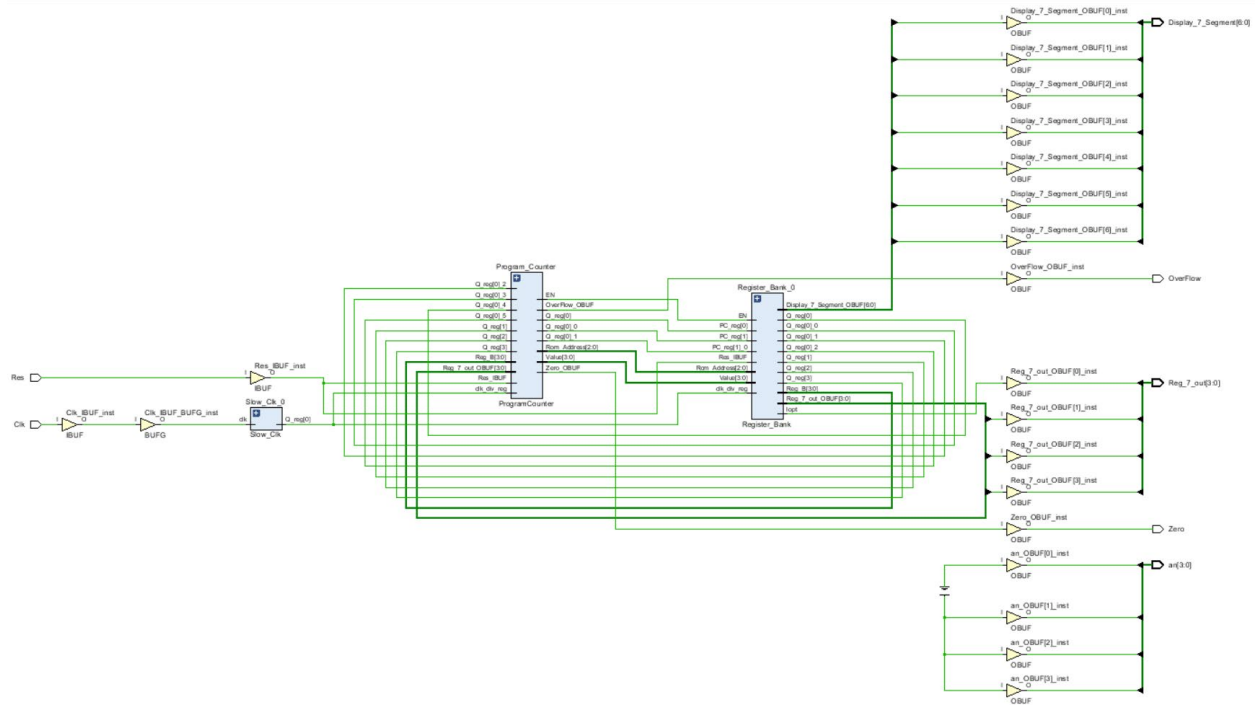

11.3. Simulation File

-- Company:

-- Engineer:

--

-- Create Date: 05/15/2025 10:05:30 PM

-- Design Name:

-- Module Name: Sim_Nano_Processor - Behavioral

-- Project Name:

-- Target Devices:

-- Tool Versions:

-- Description:

--

-- Dependencies:

--

-- Revision:

-- Revision 0.01 - File Created

-- Additional Comments:

--

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL; -- Optional for counter-style clock generation
use IEEE.NUMERIC_STD.ALL;
use ieee.std_logic_textio.all;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Sim_Nano_Processor is
-- Port ( );
end Sim_Nano_Processor;

architecture Behavioral of Sim_Nano_Processor is

    -- Component declaration of the Nano_Processor
    component Nano_Processor
        Port (
            Res      : in  STD_LOGIC;
            Clk      : in  STD_LOGIC;
            Reg_7_out : out STD_LOGIC_VECTOR(3 downto 0);
            OverFlow  : out STD_LOGIC;
            Zero      : out STD_LOGIC;
            Display_7_Segment: out STD_LOGIC_VECTOR(6 downto 0)
        );
    end component;

    -- Signals to connect to the Nano_Processor ports
    signal Res      : STD_LOGIC := '1'; -- Start with reset active
    signal Clk      : STD_LOGIC := '0';
    signal Reg_7_out : STD_LOGIC_VECTOR(3 downto 0);
    signal OverFlow  : STD_LOGIC;
    signal Zero      : STD_LOGIC;
    signal Display_7_Segment: STD_LOGIC_VECTOR(6 downto 0);

```

```

constant CLK_PERIOD : time := 20 ns; -- 50 MHz clock (for simulation)

begin

    -- Instantiate the Unit Under Test (UUT)
    UUT: Nano_Processor
        Port map (
            Res => Res,
            Clk => Clk,
            Reg_7_out => Reg_7_out,
            OverFlow => OverFlow,
            Zero => Zero,
            Display_7_Segment => Display_7_Segment
        );


    -- Clock generation process
    Clk_process :process
    begin
        while true loop
            Clk <= '0';
            wait for CLK_PERIOD/2;
            Clk <= '1';
            wait for CLK_PERIOD/2;
        end loop;
    end process;

    -- Reset process
    Reset_process :process
    begin
        -- Hold reset active for first 2 clock cycles
        Res <= '1';
        wait for 2*CLK_PERIOD;
        Res <= '0'; -- Release reset
        wait;
    end process;

end Behavioral;

```

11.4. Timing Diagram

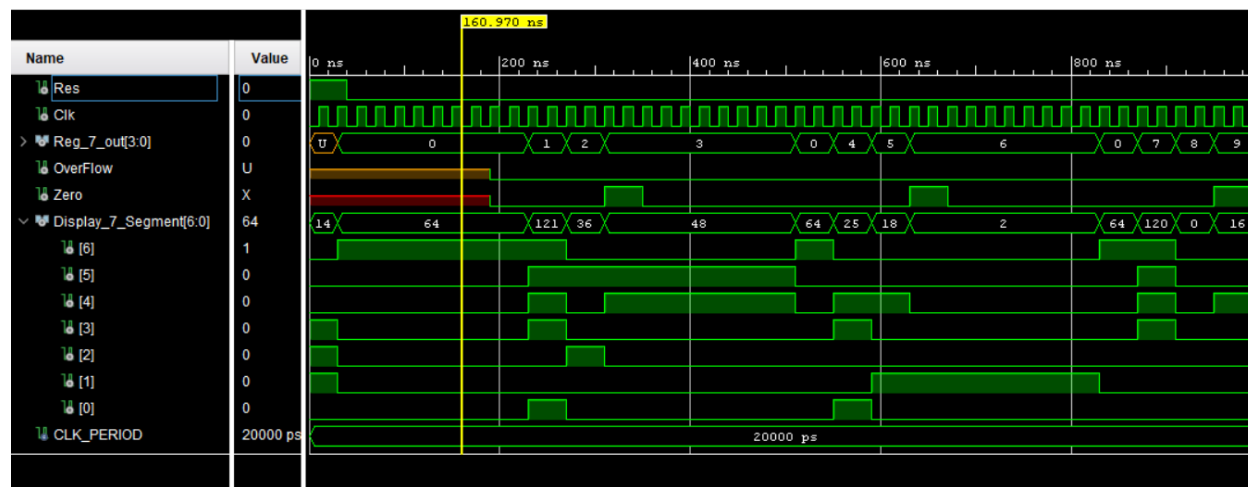

12. LUT 16_7

12.1. Design Source File

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use ieee.numeric_std.all; -- For numeric conversions

-- Entity declaration for the 16-to-7 segment LUT

entity LUT_16_7 is

Port (

 address : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit input address (0 to 15)

 data : out STD_LOGIC_VECTOR (6 downto 0) -- 7-bit output to drive seven-segment display

);

end LUT_16_7;

architecture Behavioral of LUT_16_7 is

begin

process(address)

begin

 case address is

 when "0000" => data <= "1000000"; -- 0

 when "0001" => data <= "1111001"; -- 1


 when "0010" => data <= "0100100"; -- 2

```

when "0011" => data <= "0110000"; -- 3
when "0100" => data <= "0011001"; -- 4
when "0101" => data <= "0010010"; -- 5
when "0110" => data <= "0000010"; -- 6
when "0111" => data <= "1111000"; -- 7
when "1000" => data <= "0000000"; -- 8
when "1001" => data <= "0010000"; -- 9
when "1010" => data <= "0001000"; -- A
when "1011" => data <= "0000011"; -- B
when "1100" => data <= "1000110"; -- C
when "1101" => data <= "0100001"; -- D
when "1110" => data <= "0000110"; -- E
when others => data <= "0001110"; -- F
end case;
end process;

```

12.2. Elaborate design

 

12.3. Simulation File

```
-----  
-- Company:  
-- Engineer:  
--  
-- Create Date: 05/26/2025 07:25:34 AM  
-- Design Name:  
-- Module Name: Sim_LUT_16_7 - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool Versions:  
-- Description: Testbench for LUT_16_7 - simulates a lookup table that maps  
--             4-bit binary addresses to 7-bit outputs for a seven-segment display.  
--  
-- Dependencies: Requires LUT_16_7 component definition  
--  
-- Revision:  
-- Revision 0.01 - File Created  
-- Additional Comments:  
--  
-----
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Entity for the testbench; no ports needed  
entity Sim_LUT_16_7 is  
end Sim_LUT_16_7;
```

```
architecture Behavioral of Sim_LUT_16_7 is
```

```
-- Declaration of the component under test  
component LUT_16_7  
  Port (  
    address : in  STD_LOGIC_VECTOR (3 downto 0); -- 4-bit input address (values 0 to 15)  
    data    : out STD_LOGIC_VECTOR (6 downto 0) -- 7-bit output (usually for 7-segment  
display)  
  );  
end component;
```

```
-- Signals to connect to the component's ports
signal address : STD_LOGIC_VECTOR(3 downto 0); -- Test input address
signal data    : STD_LOGIC_VECTOR (6 downto 0); -- Output from the LUT
```

```
begin
```

```
-- Instantiate the unit under test (UUT)
```

```
uut: LUT_16_7
```

```
    port map (
        address => address,
        data    => data
    );
```

```
-- Test process to apply input stimulus
```

```
process
```

```
begin
```

```
-- Apply different 4-bit address values to simulate lookup behavior
```

```
address <= "0000"; -- Expect output for 0
```

```
wait for 100 ns;
```

```
address <= "0001"; -- Expect output for 1
```

```
wait for 100 ns;
```

```
address <= "0010"; -- Expect output for 2
```

```
wait for 100 ns;
```

```
address <= "0011"; -- Expect output for 3
```

```
wait for 100 ns;
```

```
address <= "0100"; -- Expect output for 4
```

```
wait for 100 ns;
```

```
address <= "0101"; -- Expect output for 5
```

```
wait for 100 ns;
```

```
address <= "0110"; -- Expect output for 6
```

```
wait for 100 ns;
```


```
address <= "0111"; -- Expect output for 7
```

```
wait; -- End of simulation (no time delay, simulation halts here)
```

end process;

end Behavioral;

12.4. Timing Diagram

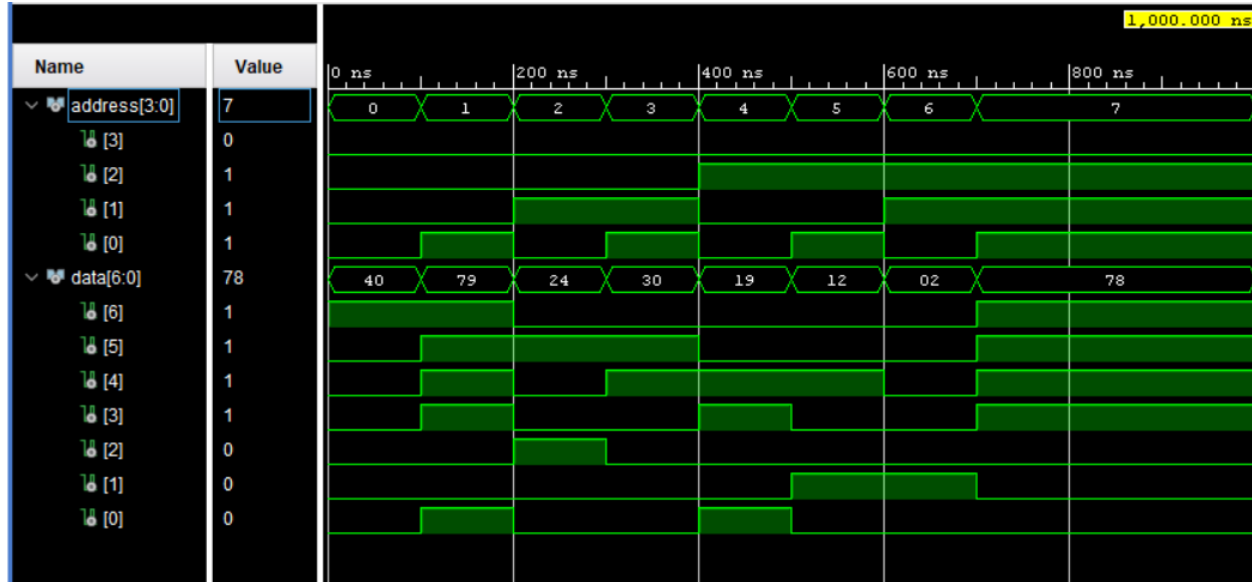

13. Rom Address Select (3 bit adder and Mux 2 way 3 bit)

13.1. Design Source File

-- Company:

-- Engineer:

-- Create Date: 14.05.2025 14:43:41

-- Design Name:

-- Module Name: 2_Way_3_Bit_Mux - Behavioral

-- Project Name:

-- Target Devices:

-- Tool Versions:

-- Description: A 2-to-1 multiplexer for 3-bit inputs. Selects between input A and B

-- based on select signal S and assigns the result to output Y.

-- Dependencies: None

-- Revision:

-- Revision 0.01 - File Created

-- Include standard logic library

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;

-- Entity declaration for the both 2-Way 3-Bit Multiplexer and 3 bit adder to select between Jump Address and next Address

entity Rom_Address_Select is

Port (

A : in unsigned(2 downto 0); -- 3-bit input vector A

B : in unsigned (2 downto 0); -- 3-bit input vector B

S : in STD_LOGIC; -- 1-bit select signal

Y : out unsigned (2 downto 0) -- 3-bit output vector Y

);

end Rom_Address_Select;

-- Architecture that defines the behavior of the multiplexer


architecture Behavioral of Rom_Address_Select is

begin

```
-- Multiplexer logic:
-- When select signal S = '1', output Y is assigned input A
-- When select signal S = '0', output Y is assigned input B incremented by 1
Y <= A when (S='1') else B + 1;
```

end Behavioral;

13.2. Elaborate design

 

13.3. Simulation File

```
-- Company:
-- Engineer:
-- Create Date: 05/26/2025 07:11:55 AM
-- Design Name:
-- Module Name: Sim_Rom_Address_Select - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description: Testbench for Rom_Address_Select module
```

-- Dependencies: Requires the Rom_Address_Select component

-- Revision:

-- Revision 0.01 - File Created

-- Additional Comments:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL; -- Required for using 'unsigned' type and arithmetic

-- Entity declaration for the testbench

entity Sim_Rom_Address_Select is

-- No ports are required for the testbench

end Sim_Rom_Address_Select;

architecture Behavioral of Sim_Rom_Address_Select is

-- Declaration of the component under test

component Rom_Address_Select

Port (

A : in unsigned(2 downto 0); -- 3-bit input address A

B : in unsigned(2 downto 0); -- 3-bit input address B

S : in STD_LOGIC; -- Select signal (if '0' select A, else select B)

Y : out unsigned(2 downto 0) -- 3-bit output address Y

);

end component;

```

-- Internal signals to connect to the DUT (Device Under Test)
signal A, B, Y : unsigned(2 downto 0); -- 3-bit unsigned vectors
signal S : STD_LOGIC;                -- Select signal

begin

-- Instantiation of the Rom_Address_Select module
 uut: Rom_Address_Select
  port map (
    A => A,
    B => B,
    S => S,
    Y => Y
  );

-- Test process to apply stimulus to the module
process
begin
  -- Initial inputs
  A <= "110"; -- Set A to 6
  B <= "000"; -- Set B to 0
  S <= '0';   -- Select B (Y should become B = "000")
  wait for 100 ns;

  -- Change value of B while S is still '0'
  B <= "011"; -- Set B to 3 (Y should be B = "011")
  wait for 100 ns;

```

```

-- Change S to select A instead (Y should become A = "110")
S <= '1';    -- Now select A (Y should become "110")


wait;

end process;

```

end Behavioral;

13.4. Timing Diagram

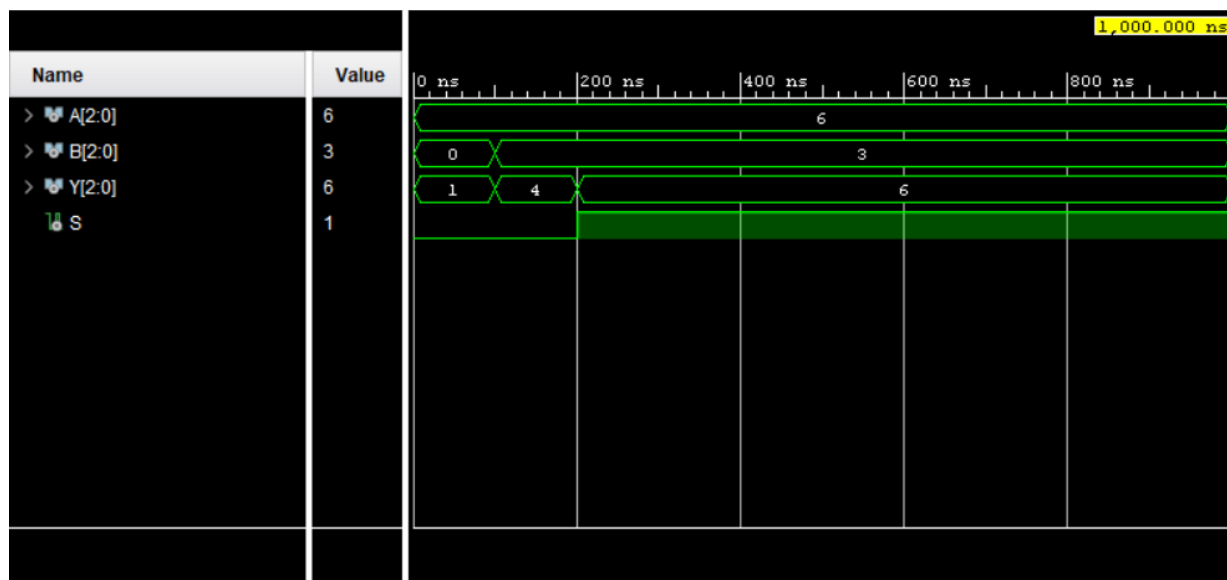

Optimization

Slow Clock

The code uses the most significant bit (MSB) of a 26-bit counter (counter(25)) as the divided clock signal. By using the MSB instead of comparing the counter to a fixed value and toggling the signal, we can generate a square wave at a frequency of $\text{Clk_in} / 2^{26}$. This approach is beneficial because it conserves logic resources by eliminating the need for complex conditional logic or additional flip-flops.

Program Counter

We utilized the UNSIGNED type from IEEE.NUMERIC_STD for arithmetic operations and value management. This approach eliminates type mismatch issues and casting that occur with STD_LOGIC_VECTOR, facilitating efficient synthesis and simulation with native numeric behavior.

Mux 2 Way 3-Bit and 3-Bit Adder (Rom_Address_select)

`Y <= A when (S='1') else B + 1;`

The entire multiplexer (MUX) logic is implemented in a single line using a conditional signal assignment. This approach minimizes logic by avoiding extra processes or nested if statements, promoting combinational synthesis and clear timing. It allows synthesis tools to easily infer a MUX and an adder.

Additionally, we have included a 3-bit adder to further reduce combinational logic. We utilize unsigned integers to directly apply the addition operator (+) to increment the input by 1.

Register Bank

case (I) is

```
when "000" => Y <= "00000001"; -- Output 0 active
when "001" => Y <= "00000010"; -- Output 1 active
when "010" => Y <= "00000100"; -- Output 2 active
when "011" => Y <= "00001000"; -- Output 3 active
when "100" => Y <= "00010000"; -- Output 4 active
when "101" => Y <= "00100000"; -- Output 5 active
when "110" => Y <= "01000000"; -- Output 6 active
when others => Y <= "10000000"; -- Covers "111" case: Output 7 active
```

end case;

We used a case statement to decode the 3-bit input in Register Bank 3 to an 8-decoder. This approach synthesizes efficiently into logic, typically resulting in a decoder tree. It allows synthesis tools to infer minimal logic paths more easily and leads to cleaner, more maintainable code compared to using a series of if-else statements.

In the register within the register bank, we chose not to use 4 D Flip-Flops for data storage. Instead, we directly assigned the data upon the rising edge of the clock signal. This method helps minimize the use of logic components.

Adder/Subtractor Unit

We combined addition and subtraction using a single adder block by modifying the inputs based on the ADD_SUB control signal. This approach saves hardware resources by avoiding separate adder and subtractor modules and implements subtraction using:

```
A_mod <= A when (ADD_SUB = '0') else not(A);
```

```
B_mod <= B when (ADD_SUB = '0') else (others => '0');
```

```
temp_sum <= ('0' & unsigned(A_mod)) + unsigned(B_mod) + ("0000" & ADD_SUB);
```

We did not use the RCA 4 to add 4-bit numbers, which helps minimize the use of logic expressions.

Constrain File

```
## This file is a general .xdc for the Basys3 rev B board
```

```
## To use it in a project:
```

```
## - uncomment the lines corresponding to used pins
```

```
## - rename the used ports (in each line, after get_ports) according to the top level signal names  
in the project
```

```
## Clock signal
```

```
set_property PACKAGE_PIN W5 [get_ports Clk]
```

```
    set_property IOSTANDARD LVCMOS33 [get_ports Clk]
```

```
    create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports Clk]
```

```
## Switches
```

```
#set_property PACKAGE_PIN V17 [get_ports {sw[0]}]
```

```
    #set_property IOSTANDARD LVCMOS33 [get_ports {sw[0]}]
```

```
#set_property PACKAGE_PIN V16 [get_ports {sw[1]}]
```

```
    #set_property IOSTANDARD LVCMOS33 [get_ports {sw[1]}]
```

```
#set_property PACKAGE_PIN W16 [get_ports {sw[2]}]
```

```
    #set_property IOSTANDARD LVCMOS33 [get_ports {sw[2]}]
```

```
#set_property PACKAGE_PIN W17 [get_ports {sw[3]}]
```

```
    #set_property IOSTANDARD LVCMOS33 [get_ports {sw[3]}]
```

```

#set_property PACKAGE_PIN W15 [get_ports {sw[4]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {sw[4]}]
#set_property PACKAGE_PIN V15 [get_ports {sw[5]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {sw[5]}]
#set_property PACKAGE_PIN W14 [get_ports {sw[6]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {sw[6]}]
#set_property PACKAGE_PIN W13 [get_ports {sw[7]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {sw[7]}]
#set_property PACKAGE_PIN V2 [get_ports {sw[8]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {sw[8]}]
#set_property PACKAGE_PIN T3 [get_ports {sw[9]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {sw[9]}]
#set_property PACKAGE_PIN T2 [get_ports {sw[10]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {sw[10]}]
#set_property PACKAGE_PIN R3 [get_ports {sw[11]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {sw[11]}]
#set_property PACKAGE_PIN W2 [get_ports {sw[12]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {sw[12]}]
#set_property PACKAGE_PIN U1 [get_ports {sw[13]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {sw[13]}]
#set_property PACKAGE_PIN T1 [get_ports {sw[14]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {sw[14]}]
#set_property PACKAGE_PIN R2 [get_ports {sw[15]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {sw[15]}]

```

LEDs

```

set_property PACKAGE_PIN U16 [get_ports {Reg_7_out[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Reg_7_out[0]}]
set_property PACKAGE_PIN E19 [get_ports {Reg_7_out[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Reg_7_out[1]}]
set_property PACKAGE_PIN U19 [get_ports {Reg_7_out[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Reg_7_out[2]}]
set_property PACKAGE_PIN V19 [get_ports {Reg_7_out[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Reg_7_out[3]}]
#set_property PACKAGE_PIN W18 [get_ports {led[4]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {led[4]}]
#set_property PACKAGE_PIN U15 [get_ports {led[5]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {led[5]}]
#set_property PACKAGE_PIN U14 [get_ports {led[6]}]

```



```
#set_property IOSTANDARD LVCMOS33 [get_ports {led[6]}]
#set_property PACKAGE_PIN V14 [get_ports {led[7]}]
#set_property IOSTANDARD LVCMOS33 [get_ports {led[7]}]
#set_property PACKAGE_PIN V13 [get_ports {led[8]}]
#set_property IOSTANDARD LVCMOS33 [get_ports {led[8]}]
#set_property PACKAGE_PIN V3 [get_ports {led[9]}]
#set_property IOSTANDARD LVCMOS33 [get_ports {led[9]}]
#set_property PACKAGE_PIN W3 [get_ports {led[10]}]
#set_property IOSTANDARD LVCMOS33 [get_ports {led[10]}]
#set_property PACKAGE_PIN U3 [get_ports {led[11]}]
#set_property IOSTANDARD LVCMOS33 [get_ports {led[11]}]
#set_property PACKAGE_PIN P3 [get_ports {led[12]}]
#set_property IOSTANDARD LVCMOS33 [get_ports {led[12]}]
#set_property PACKAGE_PIN N3 [get_ports {led[13]}]
#set_property IOSTANDARD LVCMOS33 [get_ports {led[13]}]
set_property PACKAGE_PIN P1 [get_ports {Zero}]
set_property IOSTANDARD LVCMOS33 [get_ports {Zero}]
set_property PACKAGE_PIN L1 [get_ports {OverFlow}]
set_property IOSTANDARD LVCMOS33 [get_ports {OverFlow}]
```

##7 segment display

```
set_property PACKAGE_PIN W7 [get_ports {Display_7_Segment[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Display_7_Segment[0]}]
set_property PACKAGE_PIN W6 [get_ports {Display_7_Segment[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Display_7_Segment[1]}]
set_property PACKAGE_PIN U8 [get_ports {Display_7_Segment[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Display_7_Segment[2]}]
set_property PACKAGE_PIN V8 [get_ports {Display_7_Segment[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Display_7_Segment[3]}]
set_property PACKAGE_PIN U5 [get_ports {Display_7_Segment[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Display_7_Segment[4]}]
set_property PACKAGE_PIN V5 [get_ports {Display_7_Segment[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Display_7_Segment[5]}]
set_property PACKAGE_PIN U7 [get_ports {Display_7_Segment[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Display_7_Segment[6]}]

#set_property PACKAGE_PIN V7 [get_ports dp]
#set_property IOSTANDARD LVCMOS33 [get_ports dp]
```

```
set_property PACKAGE_PIN U2 [get_ports {an[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {an[0]}]
set_property PACKAGE_PIN U4 [get_ports {an[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {an[1]}]
set_property PACKAGE_PIN V4 [get_ports {an[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {an[2]}]
set_property PACKAGE_PIN W4 [get_ports {an[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {an[3]}]
```

##Buttons

```
set_property PACKAGE_PIN U18 [get_ports Res]
    set_property IOSTANDARD LVCMOS33 [get_ports Res]
#set_property PACKAGE_PIN T18 [get_ports btnU]
    #set_property IOSTANDARD LVCMOS33 [get_ports btnU]
#set_property PACKAGE_PIN W19 [get_ports btnL]
    #set_property IOSTANDARD LVCMOS33 [get_ports btnL]
#set_property PACKAGE_PIN T17 [get_ports btnR]
    #set_property IOSTANDARD LVCMOS33 [get_ports btnR]
#set_property PACKAGE_PIN U17 [get_ports btnD]
    #set_property IOSTANDARD LVCMOS33 [get_ports btnD]
```

##Pmod Header JA

##Sch name = JA1

```
#set_property PACKAGE_PIN J1 [get_ports {JA[0]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JA[0]}]
```

##Sch name = JA2

```
#set_property PACKAGE_PIN L2 [get_ports {JA[1]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JA[1]}]
```

##Sch name = JA3

```
#set_property PACKAGE_PIN J2 [get_ports {JA[2]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JA[2]}]
```

##Sch name = JA4

```
#set_property PACKAGE_PIN G2 [get_ports {JA[3]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JA[3]}]
```

##Sch name = JA7

```
#set_property PACKAGE_PIN H1 [get_ports {JA[4]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JA[4]}]
```

```
##Sch name = JA8
#set_property PACKAGE_PIN K2 [get_ports {JA[5]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JA[5]}]
##Sch name = JA9
#set_property PACKAGE_PIN H2 [get_ports {JA[6]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JA[6]}]
##Sch name = JA10
#set_property PACKAGE_PIN G3 [get_ports {JA[7]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JA[7]}]
```

```
##Pmod Header JB
##Sch name = JB1
#set_property PACKAGE_PIN A14 [get_ports {JB[0]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JB[0]}]
##Sch name = JB2
#set_property PACKAGE_PIN A16 [get_ports {JB[1]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JB[1]}]
##Sch name = JB3
#set_property PACKAGE_PIN B15 [get_ports {JB[2]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JB[2]}]
##Sch name = JB4
#set_property PACKAGE_PIN B16 [get_ports {JB[3]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JB[3]}]
##Sch name = JB7
#set_property PACKAGE_PIN A15 [get_ports {JB[4]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JB[4]}]
##Sch name = JB8
#set_property PACKAGE_PIN A17 [get_ports {JB[5]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JB[5]}]
##Sch name = JB9
#set_property PACKAGE_PIN C15 [get_ports {JB[6]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JB[6]}]
##Sch name = JB10
#set_property PACKAGE_PIN C16 [get_ports {JB[7]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JB[7]}]
```

```

##Pmod Header JC
##Sch name = JC1
#set_property PACKAGE_PIN K17 [get_ports {JC[0]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JC[0]}]
##Sch name = JC2
#set_property PACKAGE_PIN M18 [get_ports {JC[1]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JC[1]}]
##Sch name = JC3
#set_property PACKAGE_PIN N17 [get_ports {JC[2]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JC[2]}]
##Sch name = JC4
#set_property PACKAGE_PIN P18 [get_ports {JC[3]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JC[3]}]
##Sch name = JC7
#set_property PACKAGE_PIN L17 [get_ports {JC[4]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JC[4]}]
##Sch name = JC8
#set_property PACKAGE_PIN M19 [get_ports {JC[5]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JC[5]}]
##Sch name = JC9
#set_property PACKAGE_PIN P17 [get_ports {JC[6]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JC[6]}]
##Sch name = JC10
#set_property PACKAGE_PIN R18 [get_ports {JC[7]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JC[7]}]


##Pmod Header JXADC
##Sch name = XA1_P
#set_property PACKAGE_PIN J3 [get_ports {JXADC[0]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JXADC[0]}]
##Sch name = XA2_P
#set_property PACKAGE_PIN L3 [get_ports {JXADC[1]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JXADC[1]}]
##Sch name = XA3_P
#set_property PACKAGE_PIN M2 [get_ports {JXADC[2]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JXADC[2]}]
##Sch name = XA4_P
#set_property PACKAGE_PIN N2 [get_ports {JXADC[3]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JXADC[3]}]

```

```
##Sch name = XA1_N
#set_property PACKAGE_PIN K3 [get_ports {JXADC[4]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JXADC[4]}]
##Sch name = XA2_N
#set_property PACKAGE_PIN M3 [get_ports {JXADC[5]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JXADC[5]}]
##Sch name = XA3_N
#set_property PACKAGE_PIN M1 [get_ports {JXADC[6]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JXADC[6]}]
##Sch name = XA4_N
#set_property PACKAGE_PIN N1 [get_ports {JXADC[7]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {JXADC[7]}]
```

##VGA Connector

```
#set_property PACKAGE_PIN G19 [get_ports {vgaRed[0]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {vgaRed[0]}]
#set_property PACKAGE_PIN H19 [get_ports {vgaRed[1]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {vgaRed[1]}]
#set_property PACKAGE_PIN J19 [get_ports {vgaRed[2]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {vgaRed[2]}]
#set_property PACKAGE_PIN N19 [get_ports {vgaRed[3]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {vgaRed[3]}]
#set_property PACKAGE_PIN N18 [get_ports {vgaBlue[0]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {vgaBlue[0]}]
#set_property PACKAGE_PIN L18 [get_ports {vgaBlue[1]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {vgaBlue[1]}]
#set_property PACKAGE_PIN K18 [get_ports {vgaBlue[2]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {vgaBlue[2]}]
#set_property PACKAGE_PIN J18 [get_ports {vgaBlue[3]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {vgaBlue[3]}]
#set_property PACKAGE_PIN J17 [get_ports {vgaGreen[0]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {vgaGreen[0]}]
#set_property PACKAGE_PIN H17 [get_ports {vgaGreen[1]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {vgaGreen[1]}]
#set_property PACKAGE_PIN G17 [get_ports {vgaGreen[2]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {vgaGreen[2]}]
#set_property PACKAGE_PIN D17 [get_ports {vgaGreen[3]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {vgaGreen[3]}]
```

```
#set_property PACKAGE_PIN P19 [get_ports Hsync]
    #set_property IOSTANDARD LVCMOS33 [get_ports Hsync]
#set_property PACKAGE_PIN R19 [get_ports Vsync]
    #set_property IOSTANDARD LVCMOS33 [get_ports Vsync]
```

##USB-RS232 Interface

```
#set_property PACKAGE_PIN B18 [get_ports RsRx]
    #set_property IOSTANDARD LVCMOS33 [get_ports RsRx]
#set_property PACKAGE_PIN A18 [get_ports RsTx]
    #set_property IOSTANDARD LVCMOS33 [get_ports RsTx]
```

##USB HID (PS/2)

```
#set_property PACKAGE_PIN C17 [get_ports PS2Clk]
    #set_property IOSTANDARD LVCMOS33 [get_ports PS2Clk]
    #set_property PULLUP true [get_ports PS2Clk]
#set_property PACKAGE_PIN B17 [get_ports PS2Data]
    #set_property IOSTANDARD LVCMOS33 [get_ports PS2Data]
    #set_property PULLUP true [get_ports PS2Data]
```

##Quad SPI Flash

##Note that CCLK_0 cannot be placed in 7 series devices. You can access it using the ##STARTUPE2 primitive.

```
#set_property PACKAGE_PIN D18 [get_ports {QspiDB[0]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {QspiDB[0]}]
#set_property PACKAGE_PIN D19 [get_ports {QspiDB[1]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {QspiDB[1]}]
#set_property PACKAGE_PIN G18 [get_ports {QspiDB[2]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {QspiDB[2]}]
#set_property PACKAGE_PIN F18 [get_ports {QspiDB[3]}]
    #set_property IOSTANDARD LVCMOS33 [get_ports {QspiDB[3]}]
#set_property PACKAGE_PIN K19 [get_ports QspiCSn]
    #set_property IOSTANDARD LVCMOS33 [get_ports QspiCSn]
```

Workload Distribution

Wikramaratna S. I. P.

... Final Nano Processor Design

... Register Bank

... Instruction Decoder

... LUT_16_7

de Silva N. N. B.

... Adder Subtractor 4 bit unit

... Program Counter

... Presentation

Bandara S. A. N. K.

... Mux 2 way 4 bit

... Mux 8 way 4 bit

... Lab Report

Padmasiri G.R.H.D.

... Rom Address Select

... Program Rom

Difficulties we face

During the development of our nanoprocessor, we encountered several technical and collaborative challenges. Below are the key difficulties we faced and how we addressed them:

1.Port Connection Issues

In the initial stages of the project, we faced difficulties in establishing proper connections between ports. Although the ports were connected physically, the communication was not functioning as expected due to incorrect configurations. After multiple attempts and adjustments, we were eventually able to establish the connections correctly.

2.High Utilization of Lookup Tables (LUTs)

At the beginning, our design resulted in a very high usage of lookup tables, which affected performance and scalability. We carried out several rounds of optimization, including logic simplification and resource sharing. Through these efforts, we successfully reduced LUT usage by more than 50%.

3.File Sharing and Version Control Issues

Initially, we shared project files using WhatsApp. However, this method led to multiple problems, such as the presence of duplicate files and corrupted or outdated versions. To resolve this, we created a GitHub repository, which significantly streamlined collaboration. Using GitHub enabled better version control, easier file sharing, and efficient distribution of tasks among team members.

4.Missing Components in Development Machines

At times, certain necessary software components or tools were missing from the development environments on some team members' machines. These issues were resolved collaboratively using GitHub, where updated dependencies and installation guides were made accessible to everyone, ensuring consistency across all development systems.

Conclusion

The successful completion of the Nano Processor lab project has greatly enhanced our understanding of digital system design and the practical implementation of processor architecture. Throughout this lab course, we developed each essential component systematically—from fundamental modules like the slow clock and multiplexers to more complex systems such as the instruction decoder, register bank, and the integrated nano processor itself. This modular design approach not only reinforced theoretical concepts but also improved my skills in VHDL programming, simulation practices, and system-level thinking.

The processor's ability to accurately execute instructions such as MOVI, ADD, NEG, and JZR clearly demonstrated the correctness and functionality of the architecture and instruction decoding. Additionally, the use of a slow clock and reset mechanisms allowed for detailed, step-by-step observation of instruction execution, facilitating a deeper analysis of control signal behavior and data flow within the processor.

Overall, this project provided us with valuable hands-on experience and practical insights into the design and debugging of digital systems. It also highlighted the importance of precise planning, iterative testing, and effective collaboration in successfully realizing complex hardware systems.

Group 37

230703N – Wikramaratna S. I. P.

230126X – de Silva N. N. B.

230081D – Bandara S. A. N. K.

230453V - Padmasiri G.R.H.D.